


1. Superposition theorem
2. Thevenin theorem
3. Norton theorem
4. Maximum Power Transfer theorem

Superposition theorem: states that in a linear circuit containing more than 1 sources, a current or voltage in any element is equal to the algebraic sum of current or voltage that would have been produced by individual sources acting separately.

Steps for working:

- ① Removal of ideal voltage source means shortcircuiting.
- ② Removal of practical voltage source means replacing by an internal resistance.
- ③ Removal of ideal current source means replacing by open circuit.

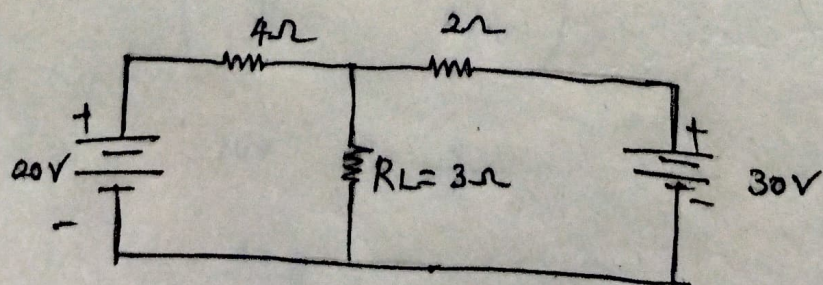
Find the current I_L , voltage V_L and power P_L in the following circuit using superposition theorem.



step 1: consider only the 20V voltage source.

step 1:

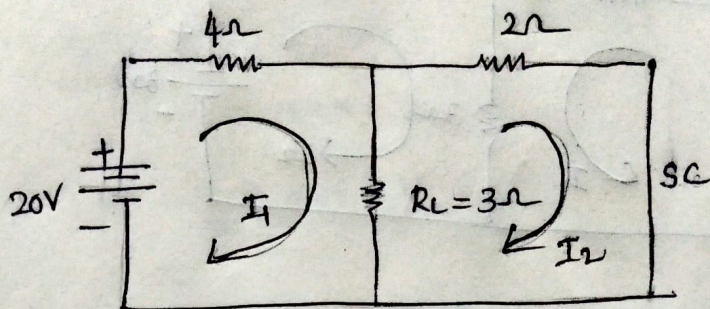Replacing 20V source by shortcircuiting the terminals and redraw the circuit.



$$[R][I] = [V]$$

By inspection :

$$\begin{pmatrix} 7 & -3 \\ -3 & 5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 20 \\ 0 \end{pmatrix}$$

$$\Delta = 35 - 9 = 26$$

$$\Delta_{I_1} = \begin{vmatrix} 20 & -3 \\ 0 & 5 \end{vmatrix} = 100$$

$$\Delta_{I_2} = \begin{vmatrix} 7 & 20 \\ -3 & 0 \end{vmatrix} = 60$$

$$I_1 = \frac{\Delta_{I_1}}{\Delta} = \frac{100}{26} = 3.846 \text{ A}$$


$$I_2 = \frac{\Delta_{I_2}}{\Delta} = \frac{60}{26} = 2.307 \text{ A}$$

$$\begin{aligned} \text{Current flow through } 3\Omega : I_1 - I_2 \\ = 3.846 - 2.307 \end{aligned}$$

$$I_{3\Omega} = \underline{\underline{1.539 \text{ A}}}$$

Consider 30 V voltage source only

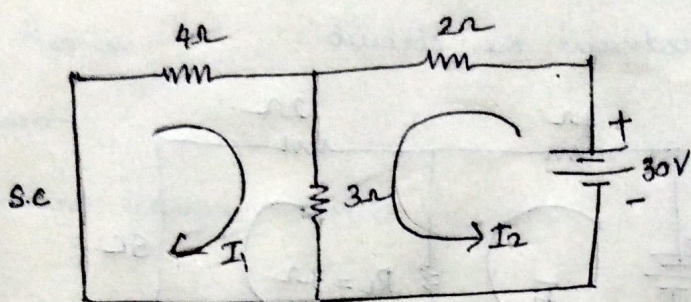Step 1: Replacing 20 V with short circuit & redraw



By inspection method

$$[R][I] = [V]$$

$$\Rightarrow \begin{pmatrix} 7 & -3 \\ +3 & 5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 0 \\ +30 \end{pmatrix}$$

$$\Rightarrow \Delta = 35 - 9 = 26$$

$$\Delta_1 = \begin{pmatrix} 0 & 3 \\ +30 & 5 \end{pmatrix} = +90$$

$$\Delta_2 = \begin{pmatrix} 7 & 0 \\ 3 & +30 \end{pmatrix} = +210$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{+210}{26} = +8.076 \text{ A}$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{-90}{26} = \underline{\underline{-3.46 \text{ A}}}$$

$$\begin{aligned} \text{Current through } 3\Omega &= +8.076 + 3.46 \\ &= \underline{\underline{+4.616 \text{ A}}} \end{aligned}$$

Step 3: The resultant current flowing through $3\ \Omega$ Resistance (R_L)

$$= 1.539 + 4.616\text{ A}$$

$$I_L = \underline{\underline{6.155\text{ A}}}$$

$$V_L = I_L R_L$$

$$= 6.155 \times 3$$


$$V_L = \underline{\underline{18.465\text{ V}}}$$

$$\text{Power } (P_L) = V_L I_L$$

$$= 18.465 \times 6.155$$

$$= \underline{\underline{113.652\text{ Watt}}}$$

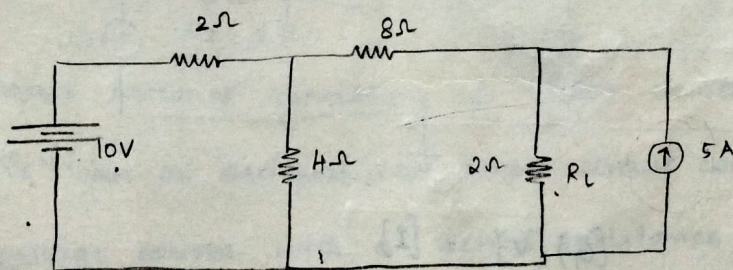
2. Find current through resistance R_L using superposition theorem



Step 1:

Consider 10V voltage source only.

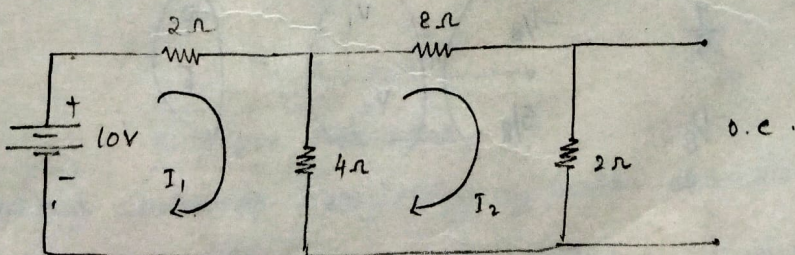Replacing the 5A current source by an open circuit.
& redrawing.



$$[R] [I] = [V]$$

$$\begin{pmatrix} 6 & -4 \\ -4 & 14 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \end{pmatrix}$$

$$\Delta = 84 - 16$$

$$= 68$$

$$\frac{16}{68} = \frac{4}{17}$$


$$\Delta I_2 = \begin{pmatrix} 6 & 10 \\ -4 & 0 \end{pmatrix} = 40$$

$$I_2 = \frac{40}{68} = \underline{\underline{0.5882}}$$

Step 2:

Consider the current source 5A only

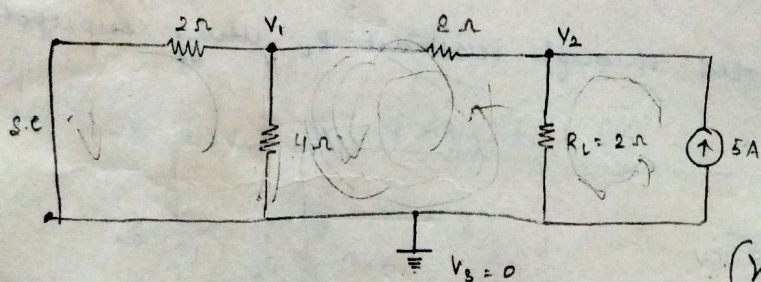Replacing the voltage source by short circuit & redraw the circuit.



$$[G][V] = [I]$$

(We should not convert into voltage source)

$$\begin{pmatrix} \frac{1}{2} + \frac{1}{8} + \frac{1}{4} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{1}{2} + \frac{1}{8} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 5 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} \frac{7}{8} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{5}{8} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 5 \end{pmatrix}$$

$$\Delta = \frac{35}{64} - \frac{1}{64} = \frac{34}{64}$$

$$\Delta V_2 = \begin{pmatrix} \frac{7}{8} & 0 \\ -\frac{1}{8} & \frac{5}{8} \end{pmatrix} = \frac{35}{8}$$

$$V_2 = \frac{35}{8} \times \frac{64}{35 \cdot 34}$$

$$\boxed{V_2 = 8.23} \text{ V}$$

$$\text{Current through } R_L = \frac{V_2}{R_L} = \frac{8.23}{2} = \underline{\underline{4 \Omega}} \quad \underline{\underline{4.117 \text{ A}}}$$

$$\text{Current} = \underline{\underline{4.117 \text{ A}}}$$

Step 3:

$$\begin{array}{r} \text{Total current } I_L = 4.1170 \\ + 0.5882 \\ \hline 4.7052 \end{array}$$

$$= \underline{\underline{4.7052 \text{ A}}}$$