

P

I

Mesh analysis (or) Loop analysis :-

- This method useful for ckt \rightarrow have many nodes and loops.
- Here one current ~~is~~ is assumed for each loop. So, one branch have more than one current.

$$V_c = -0.300$$

→ Votg balance eqn is written for each loop by applying the KVL.

→ Individual loop currents are determined by solving these equations.




for loop A-B-E-F-A,

$$-I_1 R_1 - I_1 R_3 + I_2 R_3 + V_1 = 0.$$

for loop B-C-D-E-B,

$$-I_2 R_2 - V_2 - I_2 R_3 + I_1 R_3 = 0.$$

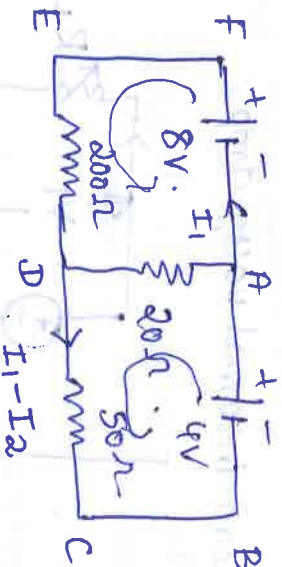1) Calculate the current in 20Ω resistor from the ckt.



$$8 - 20I_1 - 20I_2 = 0.$$

$$8 = 200I_1 + 20I_2. \quad \text{--- (1)}$$

$$-4 + 50(I_1 - I_2) - 20I_2 = 0.$$

from loop ABCDA,

$$50I_1 - 70I_2 = 4. \quad \text{--- (2)}$$

$$2 \times 4 \Rightarrow 200I_1 - 280I_2 = 16$$

$$\Rightarrow 200I_1 + 280I_2 = 8.$$

$$-300I_2 = 8, \quad I_2 = -26$$

Let current I_1 is flowing in branch FE. I_1 divides into 2 paths at node D. let I_2 be the current through DA. (i.e. 20Ω resistance) then, current through DCBA is $(I_1 - I_2)$. now, if we apply KCL at node A, current in AF is I_1 .

analysis:- \rightarrow Based on KCL. \rightarrow Used to different nodes of the circuit


\rightarrow 2 or more branches meet is called a node.

\rightarrow One node is assumed to be zero.

\hookrightarrow That is ref. node.

\rightarrow At other nodes the diff. volts are to be measured with respect to the ref.

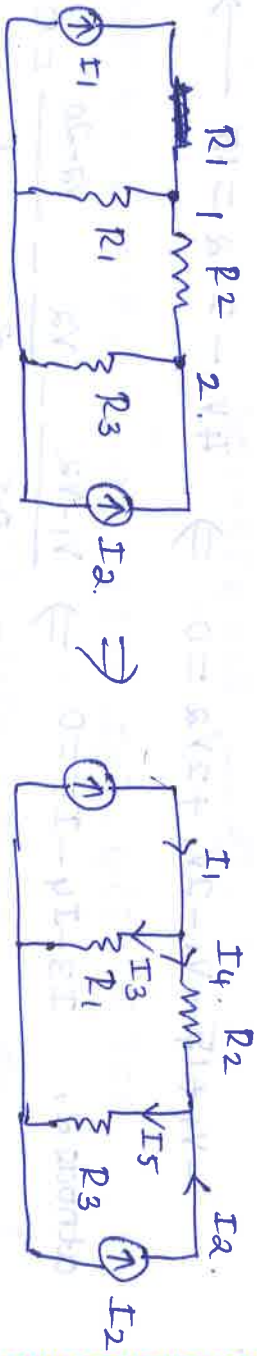\rightarrow The ref. node should be given a number zero & write eqn by KCL.



\rightarrow Let voltage at node 1 & 2 is V_1 and V_2 .

In node 1, KCL, $I_1 - I_3 - I_4 = 0 \rightarrow \textcircled{1}$


In node 2, $I_2 + I_4 - I_5 = 0 \rightarrow \textcircled{2}$

In $\textcircled{1}$, Current eqn is, $I_1 - \frac{V_1}{R_1} - \frac{(V_1 - V_2)}{R_2} = 0 \rightarrow \textcircled{3}$

$4 \textcircled{2}$, $I_2 + \frac{(V_1 - V_2)}{R_2} - \frac{V_2}{R_3} \Rightarrow 0 \rightarrow \textcircled{4}$


1) Find the current through each resistor of the circuit shown. Using

Nodal analysis.

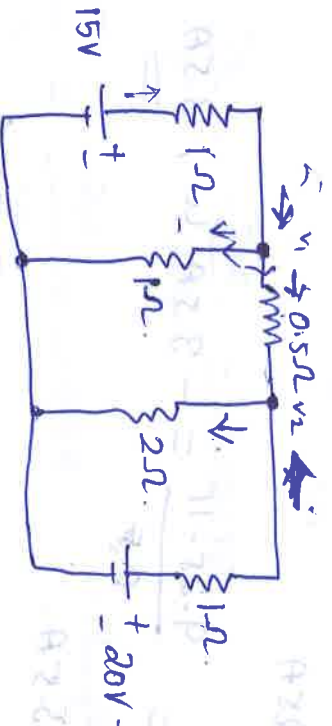

$i_1 = i_2 = i_3 = 0$
 $i_2 + i_4 - i_5 = 20$

Soln:-

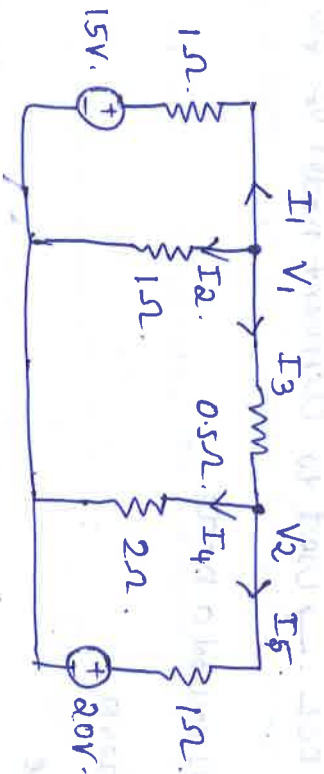

at node 1,

$$-I_1 - I_2 - I_3 = 0$$

$$-\left[\frac{V_1 - 15}{1}\right] - \left[\frac{V_1}{1}\right] - \left[\frac{V_1 - V_2}{0.5}\right] = 0$$

$$-V_1 + 15 - V_1 - 2V_1 + 2V_2 = 0 \Rightarrow 4V_1 - 2V_2 = 15 \rightarrow \text{①}$$

at node 2, $I_3 + I_4 - I_5 = 0 \Rightarrow \frac{V_1 - V_2}{0.5} - \frac{V_2}{2} - \frac{V_2 - 20}{1} = 0$

$$2V_1 - 2V_2 - 0.5V_2 - V_2 + 20 = 0$$

$$2V_1 - 3.5V_2 = -20 \rightarrow \text{②}$$

$$\text{②} \times 2 \Rightarrow 4V_1 - 7V_2 = -40$$

$$\text{①} \Rightarrow 4V_1 - 2V_2 = 15$$

$$\frac{4V_1 - 2V_2 = 15}{4V_1 - 7V_2 = -40}$$

$$5V_2 = -55 \Rightarrow V_2 = -11V$$

$$4V_1 - 2(-11) = 15 \Rightarrow 4V_1 + 22 = 15 \Rightarrow 4V_1 = -7 \Rightarrow V_1 = -1.75V$$

$$4V_1 = -7 \Rightarrow V_1 = -1.75V$$

Various currents are,

$$I_1 = \frac{V_1 - 15}{1} = \frac{-1.75 - 15}{1} = -16.75A \Rightarrow 16.75A \downarrow$$

$$V_1 = -1.75V$$


$$I_2 = \frac{V_1}{1} = -1.75A$$

$$I_3 = \frac{V_1 - V_2}{0.5} = \frac{-1.75 - (-11)}{0.5} = \frac{9.25}{0.5} = 18.5A \uparrow$$

$$I_4 = \frac{V_2 - 20}{1} = \frac{-11 - 20}{1} = -31A \Rightarrow 31A \downarrow$$

$$I_5 = \frac{V_2 - 20}{1} = \frac{-11 - 20}{1} = -31A \Rightarrow 31A \downarrow$$

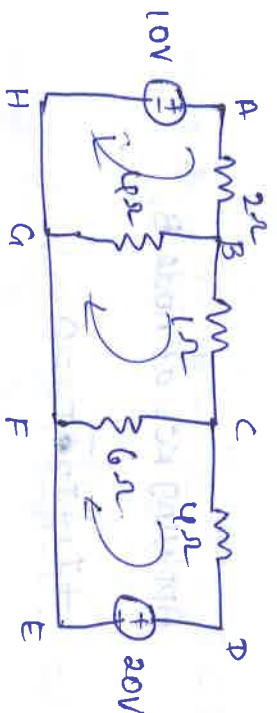rate current through 6Ω resistance using loop analysis.



Soln:-

Loop A-B-C-H-A, $-2I_1 - 4(I_1 - I_2) + 10 = 0$.

$$6I_1 - 4I_2 = 10 \quad \text{--- (1)}$$

Loop B-C-F-G-B, $-1I_2 - 6(I_2 - I_3) - 4(I_2 - I_1) = 0$

$$4I_1 - 11I_2 + 6I_3 = 0 \quad \text{--- (2)}$$

Loop C-D-E-F-C, $-4I_3 - 20 - 6(I_3 - I_2) = 0$

$$6I_2 - 10I_3 = 20 \quad \text{--- (3)}$$

Cramer's Rule,

$$\Delta = \begin{bmatrix} 6 & -4 & 0 \\ 4 & -11 & 6 \\ 0 & 6 & -10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 20 \end{bmatrix}, \Delta = 6(110 - 36) + 4(-160) = 6(74) - 160$$

Then, for I_2 ,

$$I_2 = \frac{D_2}{\Delta} = \frac{-320}{284} = -1.1267A$$


$$I_2 = \frac{D_2}{\Delta} = \frac{-320}{284} = -1.1267A$$

$$I_3 = \frac{D_3}{\Delta} = \frac{-760}{284} = -2.676A$$

Through $6\Omega = I_2 - I_3 = -1.1267 - (-2.676) = 1.5493A$ from C to D

$$V_C = -0.300$$

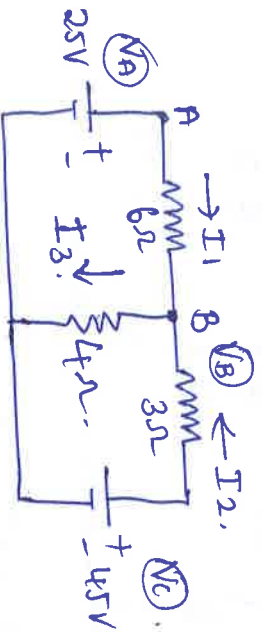1) Using node voltage analysis, obtain the currents flowing in all the resistors in the circuit shown.



Applying KCL at node B,
 $+I_1 + I_2 - I_3 = 0$.

$$I_1 = \frac{V_A - V_B}{6} = \frac{25 - V_B}{6}, \quad I_2 = \frac{V_C - V_B}{3} = \frac{45 - V_B}{3}, \quad I_3 = \frac{V_B}{4}$$

$$\left(\frac{25 - V_B}{6} \right) + \left(\frac{45 - V_B}{3} \right) - \frac{V_B}{4} = 0$$

$$\frac{25}{6} - \frac{V_B}{6} + \frac{45}{3} - \frac{V_B}{3} - \frac{V_B}{4} = 0 \quad \left| \quad \frac{V_B}{6} + \frac{V_B}{3} + \frac{V_B}{4} = \frac{25}{6} + \frac{45}{3} \right.$$

$$V_B \left(\frac{1}{6} + \frac{1}{3} + \frac{1}{4} \right) = \frac{25}{6} + \frac{45}{3} \Rightarrow V_B \left(\frac{9}{12} \right) = \frac{115}{6}$$


$$V_B = 25.56 \text{ V}$$

$$I_1 = \frac{V_A - V_B}{6} \Rightarrow \frac{25 - 25.6}{6} = -0.1 \text{ A (direction from B to A)}$$

$$I_2 = \frac{45 - 25.6}{3} = 6.47 \text{ A}$$

$$I_3 = \frac{25.6}{4} = 6.4 \text{ A}$$

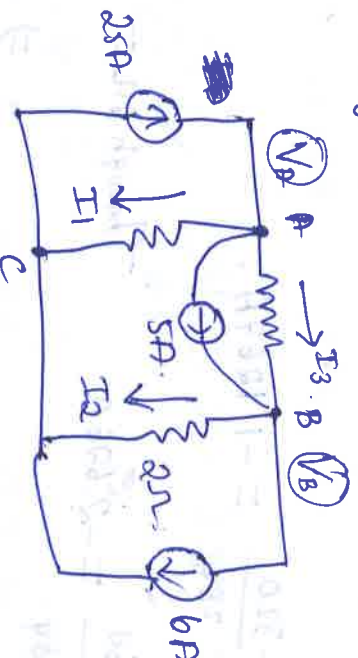2) Compute the voltage at nodes A and B in the circuit, if the reference node is C.



$$+25 - I_1 - I_3 - 5 = 0$$

$$+25 - \frac{V_A}{10} - \frac{V_A - V_B}{5} - 5 = 0$$

$$- V_A \left(\frac{1}{10} + \frac{1}{5} \right) + \frac{V_B}{5} = -20 \Rightarrow -0.3V_A + 0.2V_B = -20$$

at node B,

$$+I_3 + 5 - I_2 - 6 = 0$$

$$+ \frac{V_A - V_B}{5} - \frac{V_B}{2} = 1$$

$$\frac{V_A}{5} - V_B \left(\frac{1}{5} + \frac{1}{2} \right) = 1$$

$$0.2V_A - 0.7V_B = 1 \rightarrow (2)$$

$$(1) \times 0.2 \Rightarrow -0.06V_A + 0.04V_B = -4$$

$$(2) \times 0.3 \Rightarrow +0.06V_A - 0.21V_B = +0.3$$


$$-0.17V_B = -3.7$$

$$V_B = 21.7 \text{ Volts}$$

$$-0.3V_A + 0.2(21.7) = -20$$

$$V_A = 81.1 \text{ Volts}$$

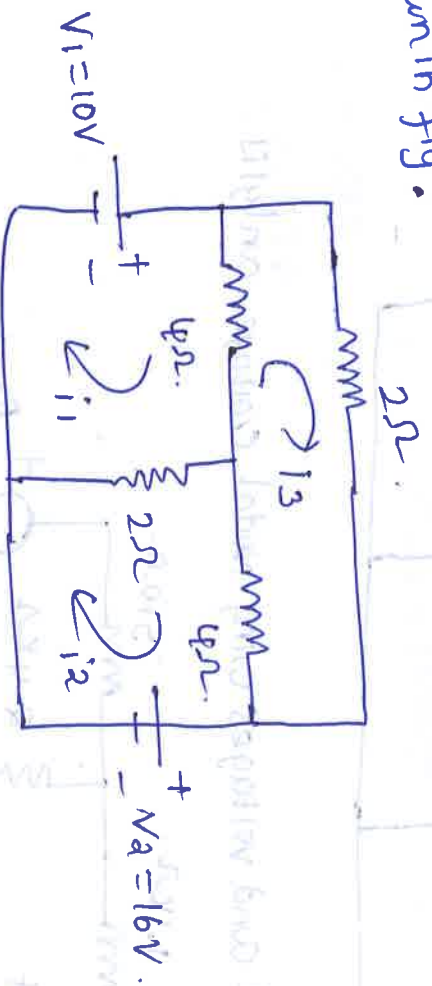* Find the Power delivered by the batteries for bridged T circuit
Shown in fig.



Soln:

$$6i_1 + 2i_2 - 4i_3 = 10$$

$$2i_1 + 6i_2 + 4i_3 = 16$$

$$-4i_1 + 4i_2 + 10i_3 = 0$$

$$\begin{bmatrix} 6 & 2 & -4 \\ 2 & 6 & 4 \\ -4 & 4 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 16 \\ 0 \end{bmatrix}$$

$$\Delta = 64$$

$$V_c = -0.300$$

$$i_1 = \frac{\Delta_{11}}{\Delta} \Rightarrow$$

$$\begin{bmatrix} 10 & 2 & -4 \\ 16 & 6 & 4 \\ 0 & 4 & 10 \end{bmatrix} = -2.125 A$$


64

$$i_2 = \frac{\Delta_{12}}{\Delta} = \frac{344}{64} = 5.375$$


Battery 1 $\Rightarrow V_{11} \Rightarrow 10(-2.125) = -21.25 W$.
 -Ve indicates power instead of delivering

Battery 2 $\Rightarrow V_{21} \Rightarrow 16(5.375) = 86 W$.

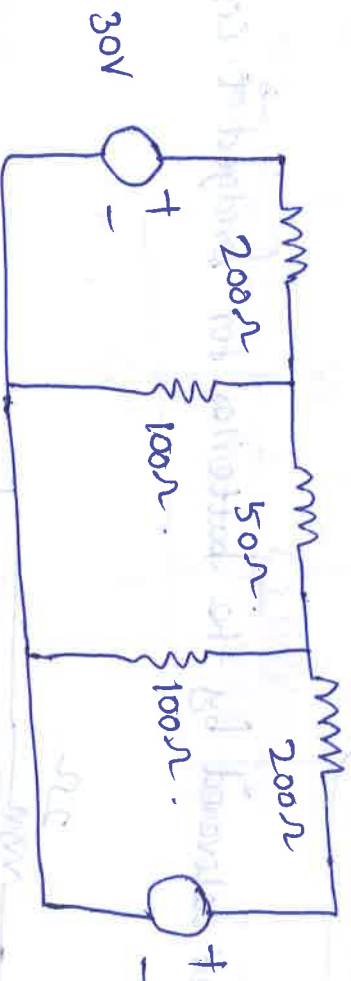
*) Using nodal analysis, determine the current in branch in the circuit.



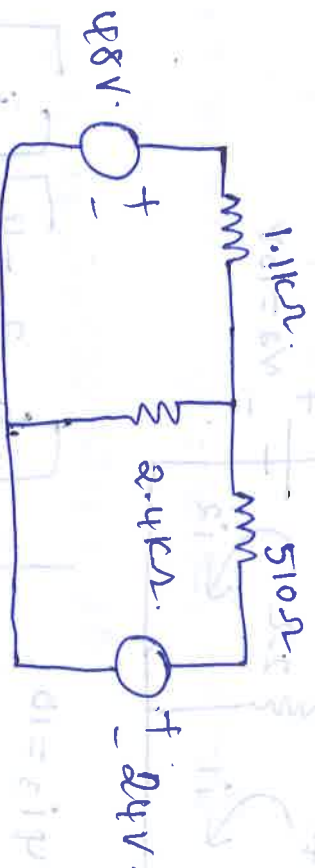*) Find current and voltages using nodal voltage analysis.



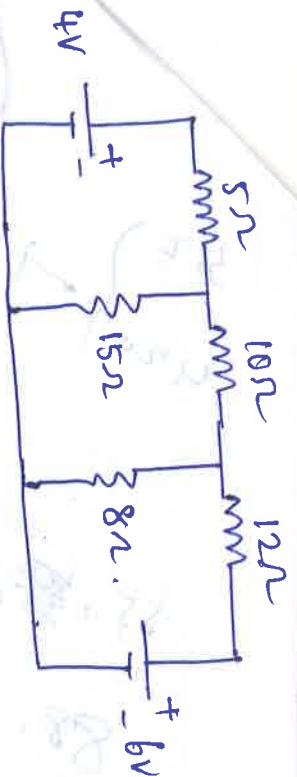* A N/w is arranged as shown in fig. Determine the value of current in the 8Ω resistor. Using mesh equation?



$$4 = 5i_1 + 15(i_1 - i_2) \Rightarrow 20i_1 - 15i_2 = 4 \quad \text{--- } \textcircled{1}$$

$$15(i_2 - i_1) + 10i_2 + 8(i_2 - i_3) = 0$$

$$15i_2 - 15i_1 + 10i_2 + 8i_2 - 8i_3 = 0$$

$$-15i_1 + 33i_2 - 8i_3 = 0 \Rightarrow 15i_1 - 33i_2 + 8i_3 = 0 \quad \text{--- } \textcircled{2}$$

$$8(i_3 - i_2) + 12i_3 = -6$$

$$8i_3 - 8i_2 + 12i_3 = -6$$

$$-8i_2 + 20i_3 = -6 \Rightarrow 8i_2 - 20i_3 = 6 \quad \text{--- } \textcircled{3}$$

$$i_1 = 0.22A$$

$$i_2 = 0.032A$$


$$i_3 = -0.287A$$

Current through 8Ω resistor $\Rightarrow 8(0.032A$

$$\Rightarrow 0.319A$$

$$V_c = -0.300$$

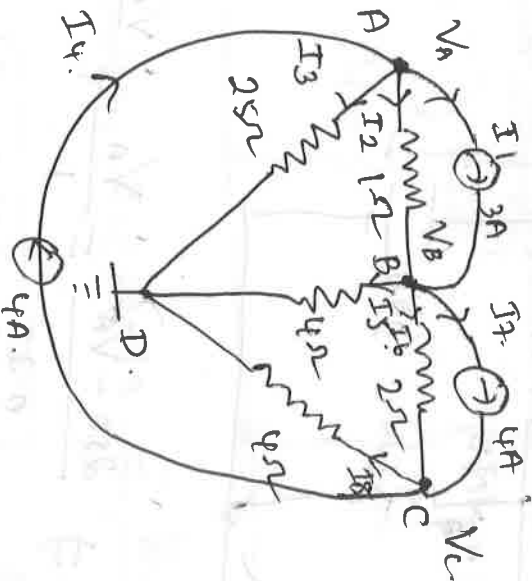power dissipated by the 4Ω resistor for the circuit shown.



Soln:-

At node 1, $\textcircled{I_1} = \textcircled{I_2} + \textcircled{I_3} + \textcircled{I_4} \Rightarrow 4 = 3 + \frac{V_A - V_B}{1\Omega} + \frac{V_A}{2.5}$

$$1 = V_A \left(1 + \frac{1}{2.5}\right) - V_B$$

$$\boxed{1 = 1.4V_A - V_B} \quad \text{--- (1)}$$

At node 2, $I_1 + I_2 = I_5 + I_6 + I_7$.

$$3 + \frac{V_A - V_B}{1} = \frac{V_B}{4} + \frac{V_B - V_C}{2} + 4$$

$$\boxed{-1 = -V_A + V_B(1.75) - 0.5V_C} \quad \text{--- (2)}$$

At node 3, $I_6 + I_7 = I_4 + I_8$

$$\frac{V_B - V_C}{2} + 4 = 4 + \frac{V_C}{4}$$

$$\boxed{0 = -0.5V_B + 0.75V_C} \quad \text{--- (3)}$$


$$\begin{bmatrix} 1.4 & -1 & 0 \\ -1 & 1.75 & -0.5 \\ 0 & -0.5 & 0.75 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \\ 0 \end{bmatrix}$$

$$V_A = 0.41$$

$$V_B = -0.42$$

$$V_C = -0.300$$
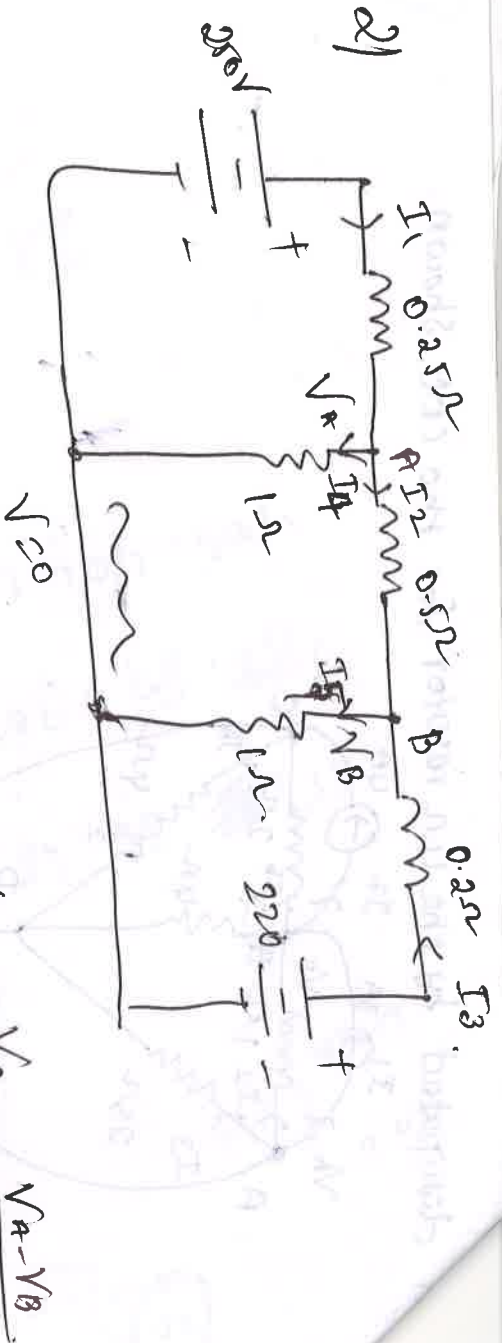
$$\begin{aligned} V_A - V_B &= 0.41 - (-0.42) = 0.83 \\ 3 + \frac{0.83}{1} &= 3 + 0.83 = 3.83 \\ -0.12 + 4 &= 3.88 \\ -0.12 + 4 &= 3.88 \end{aligned}$$



At node 1, $I_1 = I_4 + I_2$, $\Rightarrow \frac{250 - V_A}{0.25} = \frac{V_A}{1} + \frac{V_A - V_B}{0.5}$

$\frac{250}{0.25} = V_A \left(1 + \frac{1}{0.5} + \frac{1}{0.25} \right) - V_B \left(\frac{1}{0.5} \right)$

$1000 = 7V_A - 2V_B$ — (1)

At node 2, $I_2 + I_3 = I_5$

$\frac{V_A - V_B}{0.5} + \frac{220 - V_B}{0.25} = V_B$

$\frac{220}{0.25} = -V_A \left(\frac{1}{0.5} \right) + V_B \left(1 + \frac{1}{0.5} + \frac{1}{0.25} \right)$

$1100 = -2V_A + 8V_B$ — (2)


$1000 = 7V_A - 2V_B \Rightarrow \times 2 \Rightarrow 2000 = 14V_A - 4V_B$

$1100 = -2V_A + 8V_B \Rightarrow \times 1 \Rightarrow 1100 = -2V_A + 8V_B$

$900 = 52V_B$

$V_B = \frac{900}{52} = 186.5V$, $V_A = 196.15V$

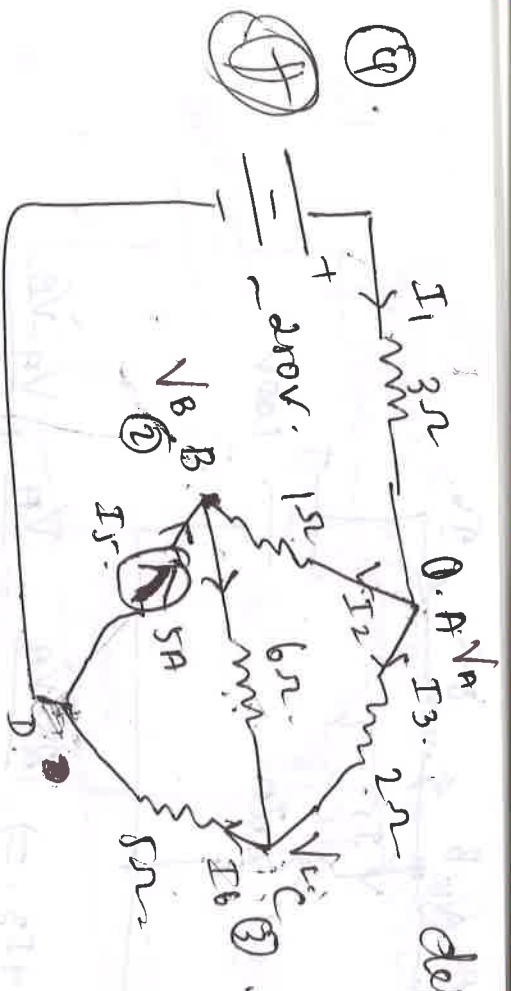$I_4 = \frac{V_A}{1\Omega} = 196.15A$, $I_5 = V_B / 1 = 186.5A$



determine P in 15Ω

Soln: At node 1, $I_1 = I_2 + I_3 \Rightarrow \frac{20 - V_A}{3} = \frac{V_A - V_B}{1} + \frac{V_A - V_C}{2}$

$83.3 = V_A (1.83) - V_B - 0.5 V_C \quad \text{--- (1)}$

At node 2, $I_2 + I_5 = I_4 \Rightarrow \frac{V_A - V_B}{1} + 5 = \frac{V_B - V_C}{6}$

$5 = -V_A + 1.167 V_B - 0.167 V_C \quad \text{--- (2)}$

At node 3, $I_3 + I_4 = I_6 \Rightarrow \frac{V_A - V_C}{2} + \frac{V_B - V_C}{6} = V_C / 5$

$0.5 V_A - 0.167 V_B + 0.867 V_C = 0 \quad \text{--- (3)}$


Cramer's Rules,

$$\begin{bmatrix} 1.83 & -1 & -0.5 \\ -1 & 1.167 & -0.167 \\ -0.5 & -0.167 & 0.867 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 83.3 \\ 5 \\ 0 \end{bmatrix}$$

$V_A = 119.6V, V_B = 118.42V$

$I_2 = \frac{V_A - V_B}{1} = 119.67 - 118.42 \Rightarrow 1.247A$

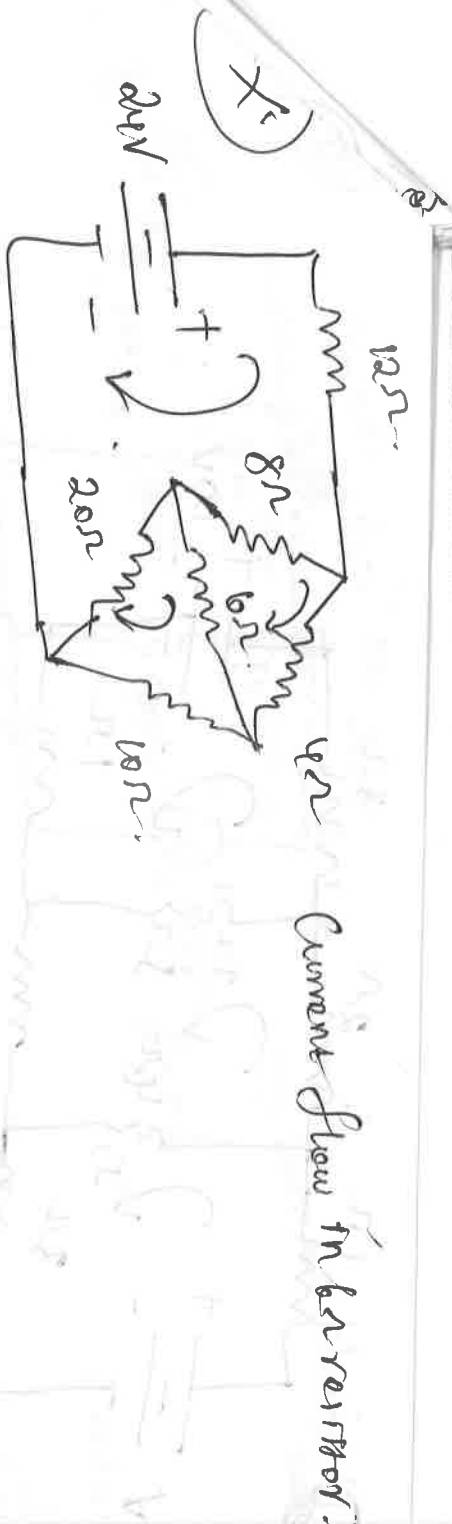$P = I_2^2 R \Rightarrow (1.247)^2 (15) = 1.55W$



Soln: in loop 1, $24 = 12I_1 + 8(I_1 - I_2) + 20(I_1 - I_3)$

$$24 = 40I_1 - 8I_2 - 20I_3 \quad \text{--- (1)}$$

in loop 2, $+8I_2 - 8I_1 + 4I_2 + 6I_2 - 6I_3 = 0$

$$-8I_1 + 18I_2 - 6I_3 = 0 \quad \text{--- (2)}$$


in loop 3, $-20I_1 - 6I_2 - 36I_3 = 0 \quad \text{--- (3)}$

$$\begin{bmatrix} 40 & -8 & -20 \\ -8 & 18 & -6 \\ -20 & -6 & 36 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 0 \end{bmatrix}, \quad \Delta = 13056$$

$$I_2 = \frac{-24(-288 - 120)}{13056} = 0$$

$$I_3 = \frac{24(48 + 360)}{13056} = 0.75 \text{ A}$$

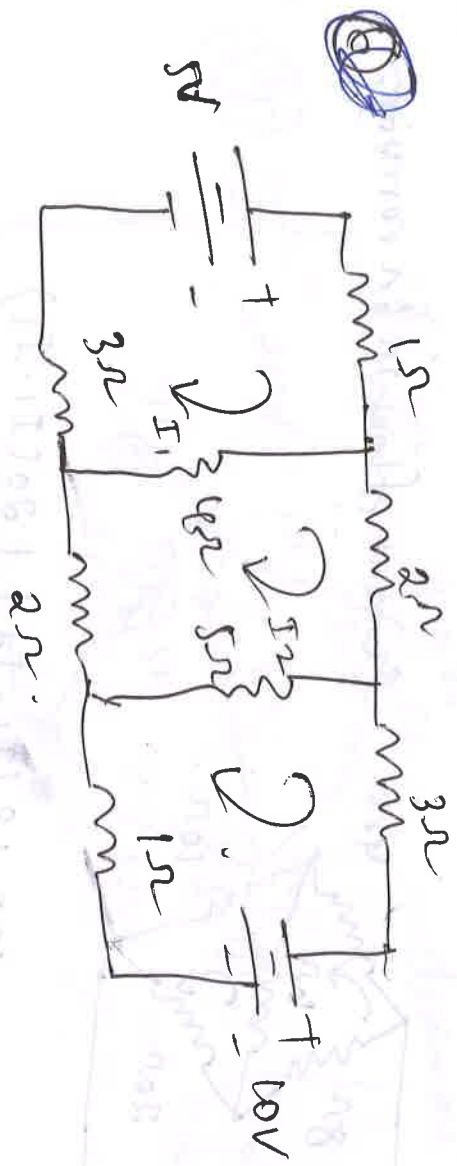Current flow through 6Ω resistor $\Rightarrow I_2 - I_1 = 0 \text{ A}$



in Loop D, $8I_1 - 4I_2 = 5$ ——— D

Loop D $8I_1 + 4I_2 - 4I_1 + 2I_2 + 5I_2 - 5I_3 = 0$


$13I_2 - 4I_1 - 5I_3 = 0$ ——— D

Loop D, $-10 = 3I_3 + 5I_3 - 5I_2 + I_1$


$-10 = 9I_3 - 5I_2$ ——— B

$$\begin{bmatrix} 8 & -4 & 0 \\ -4 & 13 & -5 \\ 0 & -5 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ -10 \end{bmatrix}$$

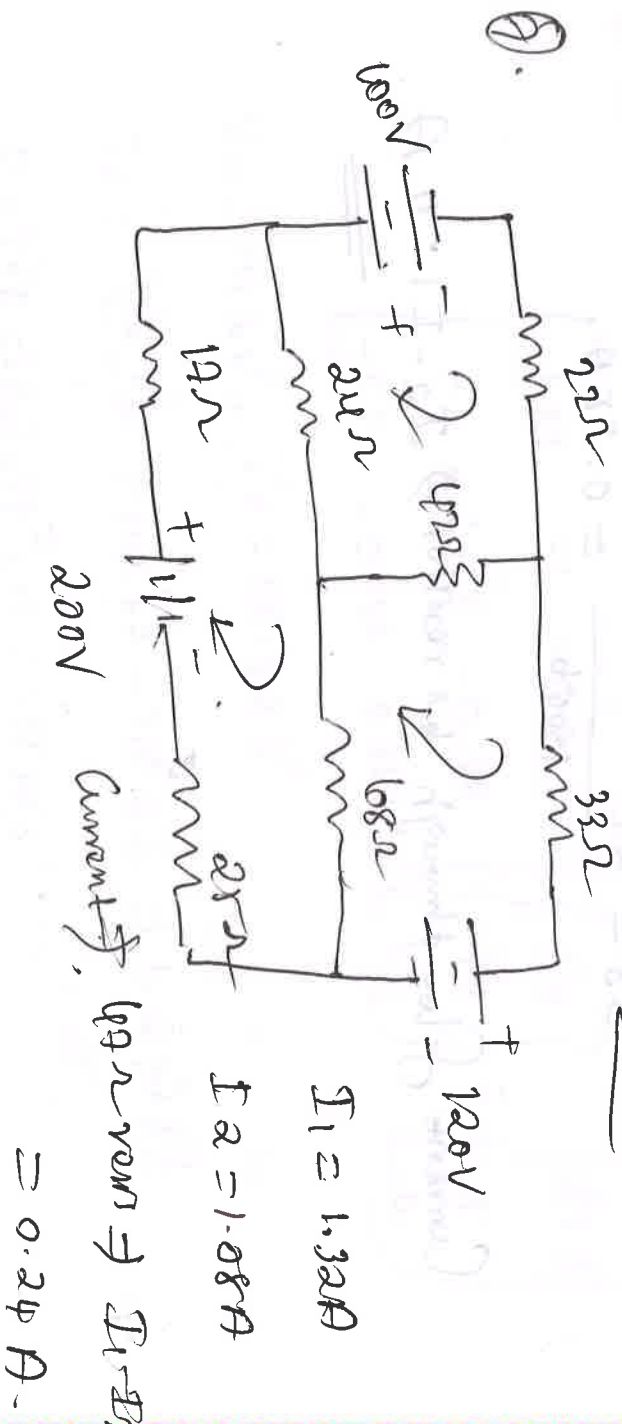$I_1 = 0.439A$
 $I_2 = -0.371A$
 $I_3 = 1.31A$


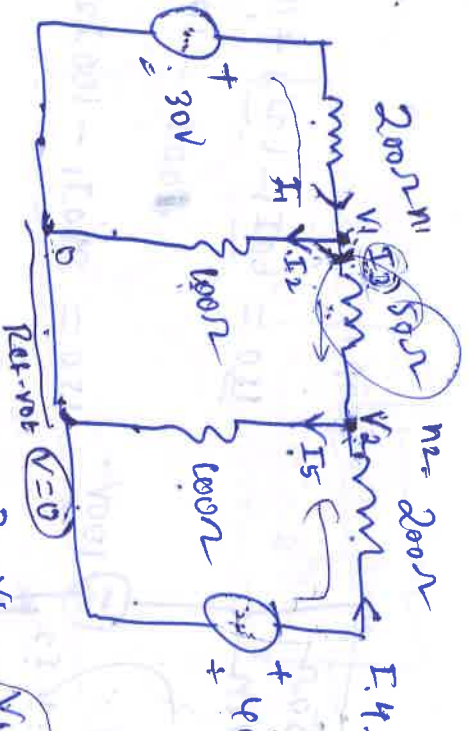
$$I = \frac{V}{R} = \frac{30 \text{ V}}{200 \Omega}$$



→ node 1, $I_1 = I_3 + I_2 \Rightarrow$

$$\frac{30 - V_1}{200} = \frac{V_1 - V_2}{50} + \frac{V_1}{100}$$

→ node 2, $I_3 + I_4 = I_5 \Rightarrow \frac{V_1 - V_2}{50} + \frac{40 - V_2}{200} = \frac{V_2}{100}$

$$\frac{30}{200} - \frac{V_1}{200} = \frac{V_1}{50} - \frac{V_2}{50} + \frac{V_1}{100} \Rightarrow \frac{30}{200} = V_1 \left(\frac{1}{50} + \frac{1}{100} + \frac{1}{200} \right) - \frac{V_2}{50}$$

$$0.15 = 0.035(V_1) - 0.02(V_2) \quad \text{--- (1)}$$

$$\frac{V_1}{50} - \frac{V_2}{50} + \frac{40}{200} - \frac{V_2}{200} = \frac{V_2}{100}$$

$$0.02V_1 - V_2 \left(\frac{1}{50} + \frac{1}{100} + \frac{1}{200} \right) = \frac{40}{200}$$

$$0.02V_1 - 0.035(V_2) = 0.2 \quad \text{--- (2)}$$

$$\textcircled{1} \times 0.02 \Rightarrow 0.0008 \quad = 0.004V_1 - 0.0004V_2$$


$$\textcircled{2} \times 0.035 \Rightarrow 0.007 \quad = 0.004V_1 - 0.001225V_2$$

$$0.010 = 0.000825V_2$$

$$V_2 = \frac{0.010}{0.000825} = 12.12 \text{ V}, \quad V_1 = 11.2 \text{ V}$$

$$I_3 = \frac{V_1 - V_2}{50} = \frac{11.2 - 12.12}{50} = -0.0184 \text{ mA}$$

2) ✓

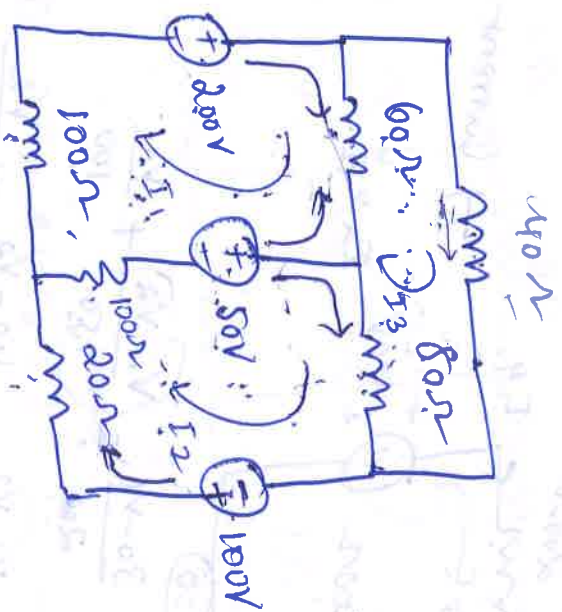

Loop 1,
 $150 = 60I_1 - 60I_3 + 100I_1 + 100I_1 - 100I_2$

$150 = 260I_1 - 100I_2 - 60I_3$

Loop 2: $150 = 100I_2 - 100I_1 + 80I_2 - 80I_3 + 20I_2$ — (2)


$150 = 200I_2 - 100I_1 - 80I_3 + 80I_3 - 80I_2$

Loop 3: $0 = 40I_3 + 60I_3 - 60I_1 - 80I_2$ — (3)

$0 = 180I_3 - 60I_1 - 80I_2$

$$\begin{bmatrix} 260 & -100 & -60 \\ -100 & 200 & -80 \\ -60 & -80 & 180 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 150 \\ 150 \\ 0 \end{bmatrix}$$

$I_1 = 1$
 $I_2 = 2$
 $I_3 = 0$

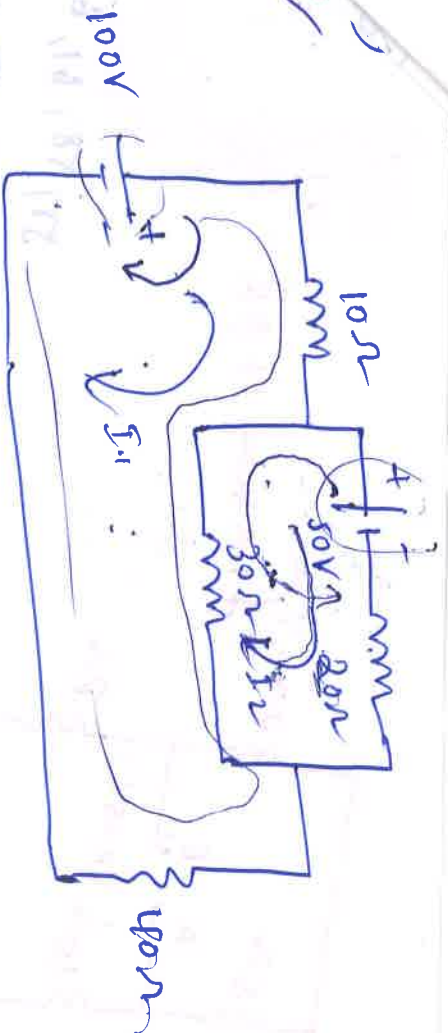

$$\text{Loop 1} \Rightarrow 100 = 40I_1 + 30I_1 - 30I_2 + 40I_1$$

$$100 = 80I_1 - 30I_2 \quad \text{--- (1)}$$

$$\text{Loop 2} \Rightarrow -50 = 20I_2 + 30I_2 - 30I_1$$

$$-50 = 50I_2 - 30I_1 \quad \text{--- (2)}$$

~~① $3000 = 2400I_1 - 900I_2$~~

~~② $4000 = -2400I_1 + 4000I_2$~~

~~$-1000 = 3100$~~

$$\text{①} = 10 = 8I_1 - 3I_2 \Rightarrow \times 5 \Rightarrow 50 = 40I_1 - 15I_2$$

$$\text{②} = -5 = -3I_1 + 5I_2 \quad \times 3 \Rightarrow -15 = -9I_1 + 15I_2$$

$$35 = 31I_1$$

$$I_1 = \frac{35}{31} = 1.12A$$

$$I_2 \Rightarrow 10 = 8(1.12) - 3I_2$$

$$10 - 8.96 = -3I_2$$

$$1.04 = -3I_2$$

$$I_2 = 0.34A$$