

R, L and C Circuits With Sinusoidal Excitation:-

→ R, L, C Circuit elements have diff. electrical properties.

R - opposes current

L - opposes changes in current

C - opposes change in voltage.

⇒ AC contains only pure values.

power factor:- → cosine angle between the voltage and current. (ϕ angle)

$$\text{power factor} = \cos\phi. P = VI \cos\phi.$$

Lagging → In Inductor, Loading → In capacitor Load.

Active (or) Real (or) True power:-

→ product of RMS value of voltage and current with cosine of the angle between them.

$$P = I_{rms} \cdot V_{rms} \cos\phi \Rightarrow VI \cos\phi. \rightarrow \text{Unit is Watts (W).}$$

Reactive power:-

→ product of RMS value of voltage & current with sine of the angle b/w them.


$$Q = V_{rms} I_{rms} \sin\phi \Rightarrow VI \sin\phi. \quad [\text{Unit is Reactive Voltampere (Var)}]$$

Apparent power :- \rightarrow Product of rms value of voltage & current is called

apparent power (S). Unit (Volt Ampere) (VA).


$$S = V_{\text{rms}} I_{\text{rms}} \quad (\text{or}) \quad S = VI.$$

$$S = \sqrt{P^2 + Q^2}.$$

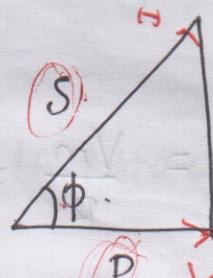


Power factor $= \frac{\text{True power}(P)}{\text{Apparent power}(S)} = \frac{VI \cos \phi}{VI} = \cos \phi$
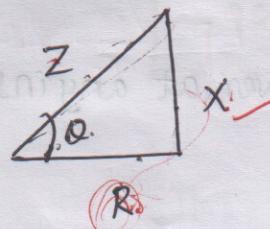
$$\text{Power factor} = \cos \phi = \frac{R}{Z} \quad (\text{Ad}) \quad (\text{hy})$$





Resistance & sinusoidal AC

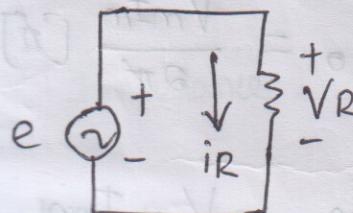\rightarrow Resistor R is connected across an alternating voltage source. In a purely resistive circuit, current i_R & voltage V_R are in phase. Since voltage & current waveforms coincide, their phasors also coincide.



(Circuit)

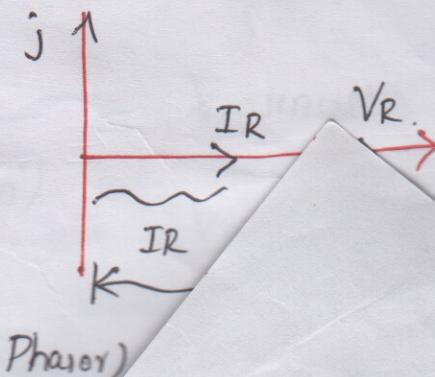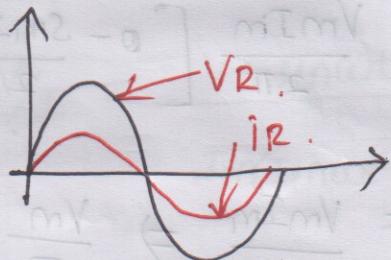


let, Applied voltage is $V = V_{\text{rms}} \sin \omega t$.

Apparent power: → Product of rms value of voltage & current is called apparent power (S). Unit (Volt Ampere) (VA).

$$S = V_{\text{rms}} I_{\text{rms}} \quad (\text{or}) \quad S = VI.$$


$$S = \sqrt{P^2 + Q^2}.$$

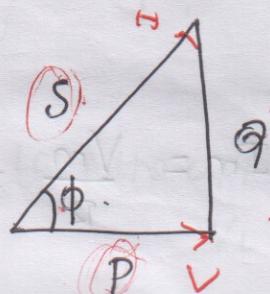

$$\sin \theta = \frac{P}{S}$$


power factor = $\frac{\text{True power}(P)}{\text{Apparent power}(S)} = \frac{VI \cos \phi}{VI} = \cos \phi$
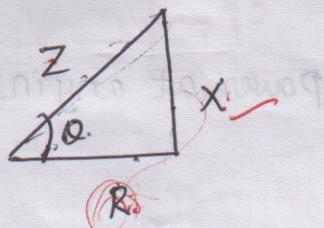
$$\text{Power factor} = \cos \phi = \frac{R}{Z} \quad (\text{Ad}) \quad (\text{hy})$$





Resistance & Sinusoidal AC

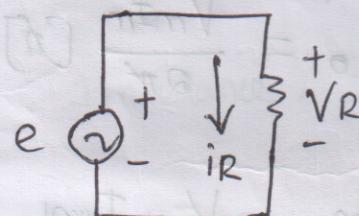→ Resistor R is connected across an alternating voltage source. In a purely resistive circuit, current i_R & voltage V_R are in phase. Since voltage & current waveforms coincide, their phasors also coincide.



(Circuit)

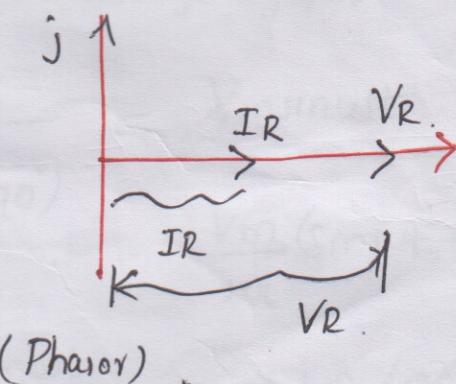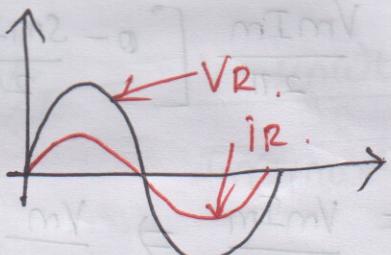

let, Applied voltage is $V = V_{\text{rms}} \sin \omega t$. ①

Resulting current has an instantaneous value, $i = V/R$.

$$i = \frac{V_m \sin \omega t}{R} = \left(\frac{V_m}{R}\right) \sin \omega t = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R} \Rightarrow \text{Peak value of current.}$$

Impedance

$$Z = V/i \Rightarrow \frac{V_m \sin \omega t}{I_m \sin \omega t} = \frac{V_m}{V_m/R} = R.$$

$\sqrt{4} I$ in each other

Power at any instant, $P = VI$

$$= (V_m \sin \omega t) (I_m \sin \omega t)$$

$$P = V_m I_m \sin^2 \omega t. \quad (\omega = \omega t)$$

Power,

$$\text{Avg. power over a cycle, } P = \frac{V_m I_m}{\pi} \int_0^\pi \sin^2 \omega t \cdot d\omega.$$

$$= \frac{V_m I_m}{2\pi} \int_0^\pi (1 - \cos 2\omega) \cdot d\omega.$$

$$= \frac{V_m I_m}{2\pi} \left[\omega - \frac{\sin 2\omega}{2} \right]_0^\pi = \frac{V_m I_m}{2\pi} \quad [if]$$




$$= \frac{V_m I_m}{2} \Rightarrow \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} \cdot I_{rms}.$$

$$P = VI \text{ Watts.}$$

power factor, \rightarrow cosine angle between Voltage and current.

$$\cos\phi = \cos 0 = 1. [\phi = 0, \text{ bcz } V \& I \text{ in phase}]$$

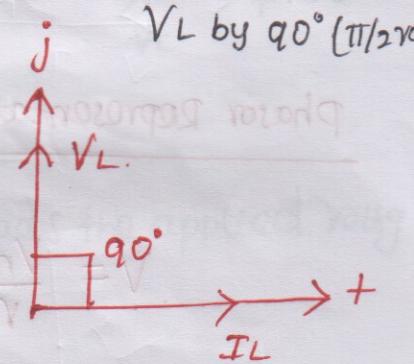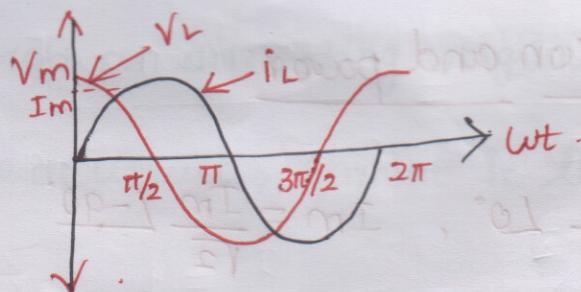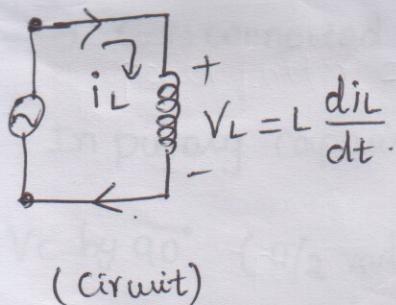Inductance and sinusoidal AC: - \rightarrow Current i_L lags the applied voltage



$$\text{Applied voltage, } V = V_m \sin \omega t \quad \text{--- (1)}$$

$$\text{current through the inductor (i), } i = \frac{1}{L} \int V dt.$$

$$= \frac{1}{L} \int V_m \sin \omega t \cdot dt = \left(\frac{V_m}{\omega L} \right) (-\cos \omega t)$$

$$i = I_m (\sin \omega t - 90^\circ) \quad \text{--- (2)}$$

from (1) & (2), current through an inductor lags the voltage by 90° .

$$\begin{aligned} \text{Impedance, } Z &= \frac{V}{I} = \frac{V_m \sin \omega t}{I_m (\sin \omega t - 90^\circ)} = \frac{V_m \sin \omega t}{\frac{V_m (\sin \omega t - 90^\circ)}{\omega L}} \\ &= \omega L \cdot \frac{\sin \omega t}{\sin(\omega t - 90^\circ)} \Rightarrow \omega L \angle 90^\circ = j \omega L \end{aligned}$$

$$Z \approx j X_L$$

$Z = \omega L \rightarrow$ inductive reactance $\leftarrow X_L$. Unit (s Ohm (Ω)).

$$X_L = \omega L = 2\pi f L, \omega = 2\pi f.$$

In a purely inductive circuit, the opposition to the flow of alternating current is called inductive reactance (X_L).

Phasor Representation and power:

$$V = \frac{V_m}{\sqrt{2}} \angle 0^\circ, I_m = \frac{I_m}{\sqrt{2}} \angle -90^\circ$$

Instantaneous power $\left\{ P = VI \right\} \Rightarrow V_m I_m \cos(\phi - \pi/2)$
(con.)

Power at any instant

$$P = -V_m I_m \sin(\phi) \text{ or } P = -V_m I_m \sin(\phi).$$

$$\text{Avg. power} = \frac{-V_m I_m}{\pi} \int_0^{\pi} (\sin \phi \cos \phi) d\phi.$$

$$= -\frac{V_m I_m}{\pi} \int_{-\pi}^{\pi} \sin 2\phi d\phi \Rightarrow \frac{V_m I_m}{2\pi} \left(\frac{\cos 2\phi}{2} \right)_0^{\pi}$$



$$P = \frac{V_m I_m}{4\pi} (\cos 2\pi - \cos 0) = 0.$$

So, pure inductor does not consume any real power.

$$\text{Power factor} = \cos \phi \neq \cos 90^\circ = 0.$$

Power factor is zero lagging.

Capacitance and Sinusoidal AC:-

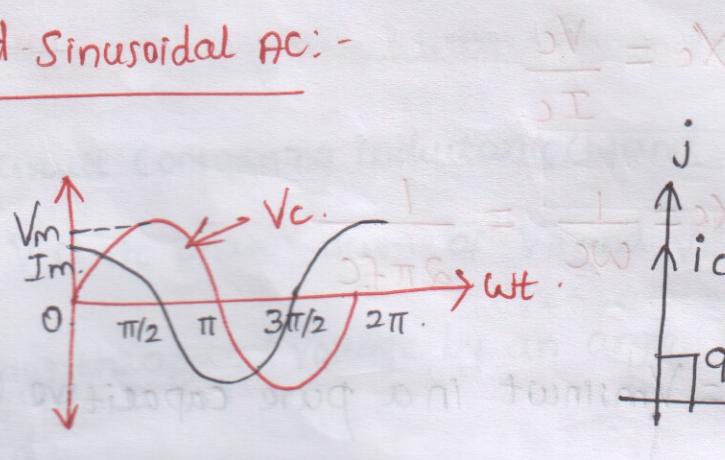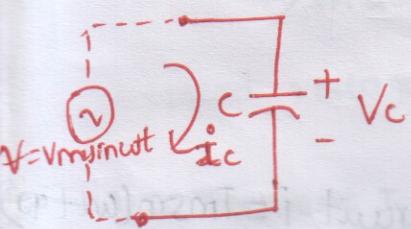

→ C is connected across an alternating Voltage Source.

→ In purely capacitive ac circuit, Current i_c leads the applied voltage V_c by 90° . ($\pi/2$ rads).

$$\text{Applied Voltage } V = V_m \sin \omega t \quad \text{---} \textcircled{1}$$

$$\text{Voltage across the capacitor is, } V = \frac{1}{C} \int i dt$$

$$\text{Current through capacitor } i = C \frac{dV}{dt}$$

$$i = C \frac{d}{dt} (V_m \sin \omega t) \Rightarrow V_m \cdot C \cdot \omega \cos \omega t$$

$$= \frac{V_m}{1/\omega C} \cdot \cos \omega t$$

$$i = +I_m \cos \omega t \Rightarrow I_m (\sin \omega t + 90^\circ)$$

$$\text{where, } I_m = \frac{V_m}{1/\omega C} = \frac{V_m}{X_C}, \text{ i.e., } X_C = 1/\omega C \rightarrow \text{Capacitive reactance in ohms.}$$

→ In purely capacitive Circuit the opposition to the flow of alternating current is called capacitive reactance.

$$X_C = \frac{V_C}{I_C}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

So, for given $V = V_m \sin \omega t$ in a pure capacitive circuit $i = I_m \sin(\omega t + 90^\circ)$
the current is leading voltage by 90° .

Phasor representation & power:

$$V = \frac{V_m}{\sqrt{2}} \angle 0^\circ \quad \text{and} \quad I = \frac{I_m}{\sqrt{2}} \angle 90^\circ$$

Power factor = $\cos 90^\circ = 0 \rightarrow$ Zero leading.

Instantaneous power (P) = $V_i = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ)$

$$\text{Avg. power} = \frac{V_m I_m}{\pi} \int_0^{\pi} \sin \omega t \cos \omega t d\omega, \quad (\omega t = \theta)$$

$$= \frac{V_m I_m}{2\pi} \int_0^{\pi} \sin 2\theta d\theta.$$

$$= -\frac{V_m I_m}{2\pi} \left[\frac{\cos 2\theta}{2} \right]_0^{\pi} = 0.$$


Thus a pure capacitor does not consume any real power.

R-L-Series AC Circuit:-


→ In ac circuit containing inductance(L) and Resistance (R), the applied voltage V is the phasor sum of V_R and V_L .

→ Current I lags the applied voltage by an angle lying between 0° and 90° .


Shown as angle ϕ .

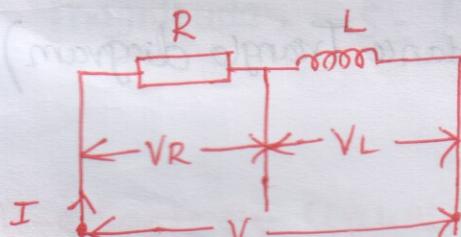


(Circuit)

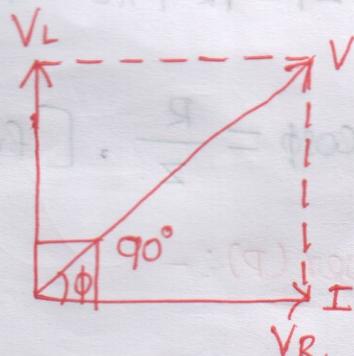


(b) phasor diagram.

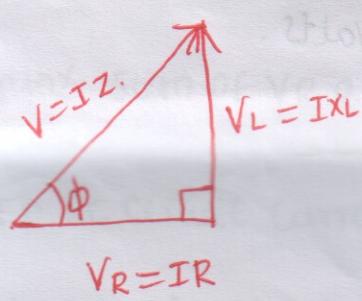

(Voltage triangle)

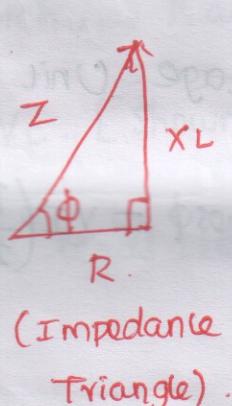

(Impedance triangle).

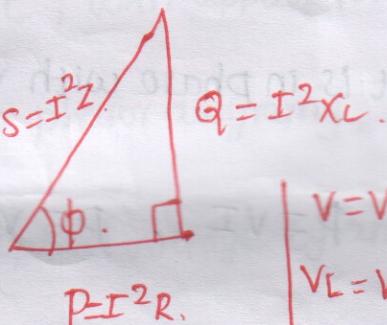

$$\begin{cases} V = V_{ms} \sin \omega t & \text{Applied voltage} \\ V_L = V_0 \sin(\omega t + 90^\circ) & \text{Voltage across inductor} \\ V_R = V_0 \sin \omega t & \text{Voltage across Resistor} \end{cases}$$

→ In a Series RL circuit the current flowing through R and L is common.

4 that taken as Reference phasor.

→ In Resistance the voltage across it V_R and current I are in phase.

→ In Inductor, voltage across it V_L leads current I by 90° .

For the R-L circuit, $|V| = \sqrt{V_R^2 + V_L^2}$.

$$\tan \phi = \frac{V_L}{V_R}, \quad \phi = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$

In an a.c circuit, the ratio applied voltage V to current I .

$$Z = V/I.$$

Impedance (Z), $Z = R + jX_L$.

$$|Z| = \sqrt{R^2 + X_L^2}, \tan\phi = \frac{X_L}{R}, \sin\phi = \frac{X_L}{Z},$$

$$\cos\phi = \frac{R}{Z}. \quad [\text{from Impedance Triangle diagram}].$$

Active (or) Real power (P):-

→ Only the Real power can be produced at the time of Current Component is in phase with voltage. Unit is Watts.

$$P = VI, P = VI \cos\phi = VI \left(\frac{R}{Z}\right)$$

$$P = \frac{V}{Z} \times I \times R.$$

$$P = I^2 R.$$

Reactive power (Q):-

→ Reactive power consumption in any circuit when a current component is in quadrature with voltage. Unit is Volt Ampere Reactive.

$$Q = V \times \text{quadrature component of current}$$

$$Q = VI \sin\phi \Rightarrow VI \frac{X_L}{Z}, Q = \frac{V}{Z} * I * V_L = I^2 X_L.$$

Apparent power (S) :-

→ It is calculated as the product of voltage and current. Unit Volt Ampere.

$$S = V * I \Rightarrow I^2 Z \Rightarrow V^2 / Z$$





$$S = P + jQ$$

Magnitude, $S = \sqrt{P^2 + Q^2}$

R-C Series AC Circuit:

→ In an a.c circuit, which has R and C, with applied voltage V is the 'phasor' sum of V_R and V_C . [shown in phasor diagram].

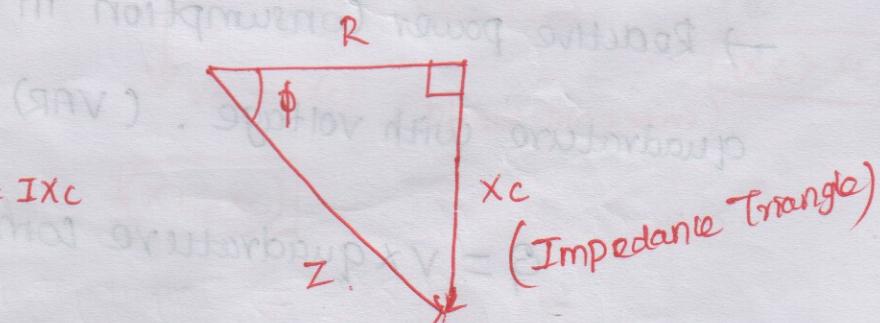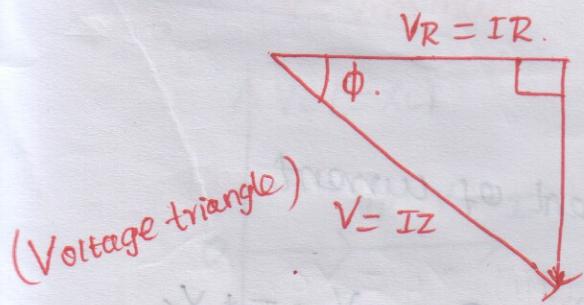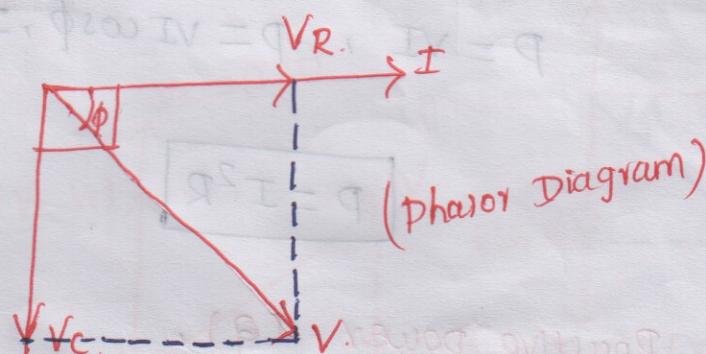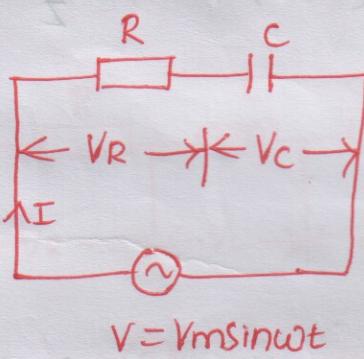→ In RC Circuit Current I leads the applied voltage by an angle lying between 0° and 90° .



In R-C circuit, $V = \sqrt{V_R^2 + V_C^2}$

$$\tan \phi = \frac{V_C}{V_R}, \quad \phi = \tan^{-1} \left(\frac{V_C}{V_R} \right)$$

Then, Impedance (Z) is, $Z = \frac{V}{I}$

from Impedance triangle ~~triangle~~ diagram, $Z = \sqrt{R^2 + X_C^2}$

$$\tan \phi = \frac{X_C}{R}; \quad \sin \phi = \frac{X_C}{Z}; \quad \cos \phi = \frac{R}{Z}$$

Active (or) Real power, (P),

→ Only the power can be consumed at the time of current is in phase with voltage. (W).

$$P = VI, \quad P = VI \cos \phi, \quad P = VI \left(\frac{R}{Z} \right), \quad P = \frac{V}{Z} * I * R$$

$$P = I^2 R$$



Reactive power, (Q),


→ Reactive power Consumption in any circuit when a current is in quadrature with voltage. (VAR)

$Q = V \times \text{quadrature component of current}$

$$Q = VI \sin \phi, \quad Q = VI \left(\frac{X_C}{Z} \right), \quad Q = \frac{V}{Z} * I * X_C$$

$$Q = I^2 X_C$$

$$P = I^2 R.$$

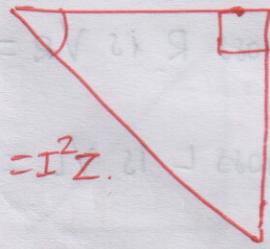

Apparent power (S),

→ product of voltage and current. $S = VI = I^2 Z \Rightarrow V^2/Z$.

$$S = P + jQ.$$

$$S = \sqrt{P^2 + Q^2}.$$

$$V_m \sin \omega t = V$$


$$(V_m - jV) + jV = V$$

$$\sqrt{(V_m - jV)^2 + j^2 V^2} = V$$



AC R-L-C Series Circuit :-

→ In ac circuit containing resistance R , inductance L , & capacitance the applied voltage V is the phasor sum of V_R , V_L and V_C . [shown in phasor diagram].

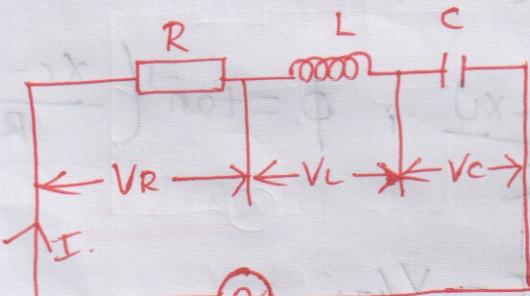→ V_C and V_L are anti-phase. i.e., displaced by 180° .



$$V = V_m \sin \omega t$$

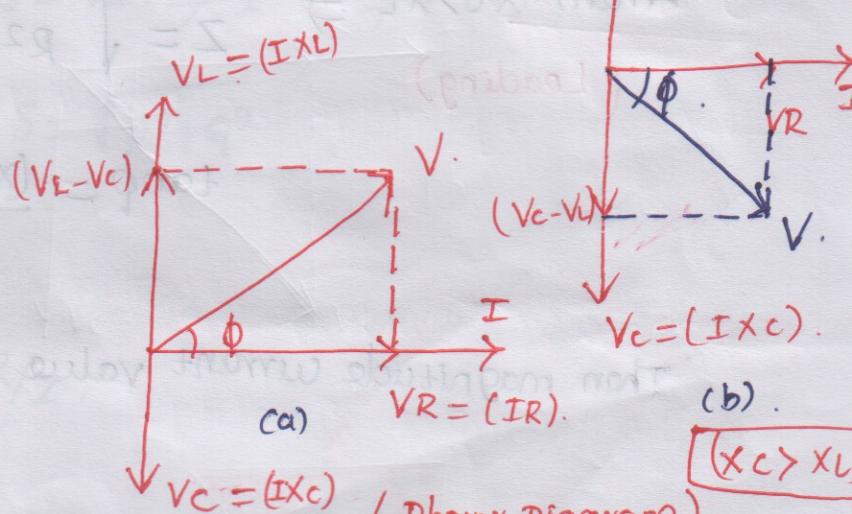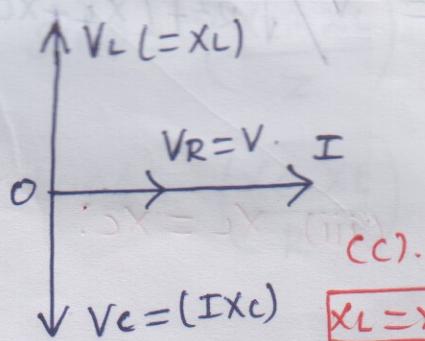

$$(XL > XC)$$

(Phasor Diagram)

$$(XL > XC)$$

(b).

$$(XC < XL)$$

(XL > XC)

(XC < XL)

(XL > XC)

(XC < XL)

→ Voltage across R is $V_R = IR \rightarrow$ in phase with current I.

→ Voltage across L is $V_L = IX_L$ $\angle 90^\circ$ → Current ~~leads~~ voltage by 90°
 $(jIX_L) \rightarrow$ voltg leads current by 90° .

→ Voltage across C is $V_C = IX_C$ $\angle -90^\circ$ → current leads voltage by 90° .
 $(-jIX_C) \rightarrow$ voltg lags current by 90° .

Applied voltage $V = V_m \sin \omega t$.

$$V = V_R + (V_L - V_C)$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

Impedance (Z) is, $Z = V/I$.

When, $X_L > X_C \Rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2}$

(Lagging)

$$\tan \phi = \frac{(X_L - X_C)}{R}, \quad \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right).$$

When, $X_C > X_L \Rightarrow$

(Leading)

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\tan \phi = \frac{(X_C - X_L)}{R}, \quad \phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

Then magnitude current value, $I = V/Z$.

$$I = \sqrt{R^2 + (X_L - X_C)^2}$$


Two conditions,

(i) $X_L > X_C \Rightarrow$ Lagging P-f (iii) $X_L = X_C$.

(ii) $X_C > X_L \Rightarrow$ Leading P-f.

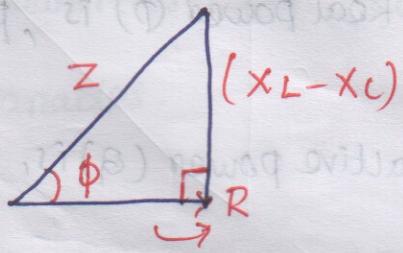(ii) $X_L > X_C$:-

In this condition, $\cos\phi = \frac{R}{Z}$.



$$\sin\phi = \left(\frac{X_L - X_C}{Z}\right)$$

$$\tan\phi = \left(\frac{X_L - X_C}{R}\right)$$

So, Real power (P) is, $P = VI$, $P = VI \cos\phi \Rightarrow VI(R/Z)$

$$P = I^2 R$$

Reactive power (Q) is, $Q = VI \sin\phi$

$$Q = V \cdot I \cdot \left(\frac{X_L - X_C}{Z}\right)$$

$$Q = I^2 (X_L - X_C)$$

Apparent power (S) is, $S = VI \neq I^2 Z \Rightarrow V^2/Z$


$$S = \sqrt{P^2 + Q^2}$$

(iii) $X_C > X_L$:-

In this condition, $\cos\phi = R/Z$,

$$\sin\phi = \left(\frac{X_C - X_L}{Z}\right)$$
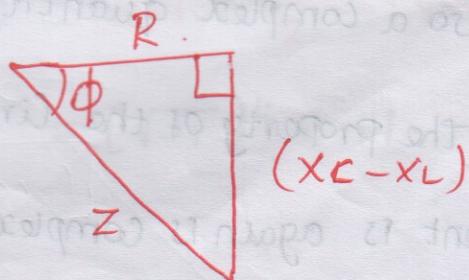
$$\tan\phi = \left(\frac{X_C - X_L}{R}\right)$$



Real power (Φ) is, $P = VI \cos \phi$ $P = I^2 R$

Reactive power (Q) is, $Q = VI \sin \phi$

$$Q = VI \cdot \left(\frac{X_C - X_L}{Z} \right) = \Phi \text{ m.s}$$

$$\boxed{Q = I^2 (X_C - X_L)} = \Phi \text{ m.f}$$

Apparent power (S) is, $S = VI$, $S = I^2 Z$, $S = V^2 / Z$.

$$S = \sqrt{P^2 + Q^2}$$

(iii) $X_L = X_C$.

→ When $X_C = X_L$, the applied voltage V and the current are in phase.

This effect is called Series resonance.