




# **21EES101J - BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

# **Unit-1**

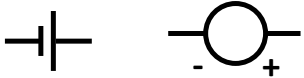
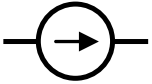

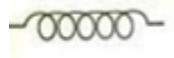
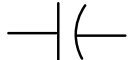
## **ELECTRIC CIRCUITS**

Electric circuits are broadly classified as Direct Current (D.C.) circuits and Alternating Current (A.C.) circuits. The following are the various elements that form electric circuits.

### D.C. Circuits

<u>Elements</u>	<u>Representation</u>
Voltage source	
Current source	
Resistor	

### A.C. Circuits


<u>Elements</u>	<u>Representation</u>
Voltage source	
Current source	
Resistor	
Inductor	
Capacitor	

We also will classified sources as **Independent** and **Dependent** sources


**Independent source** establishes a voltage or a current in a circuit without relying on a voltage or current elsewhere in the circuit

**Dependent sources** establishes a voltage or a current in a circuit whose value depends on the value of a voltage or a current elsewhere in the circuit

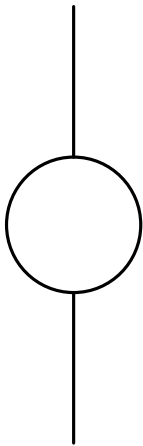We will use circle to represent **Independent source** and diamond shape to represent **Dependent sources**





**Independent source**

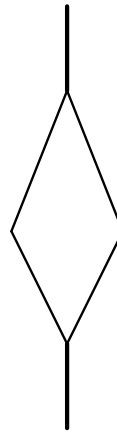

**Dependent sources**
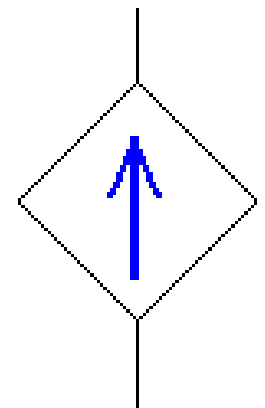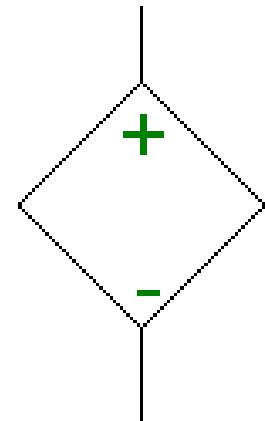
# Dependent Power Sources


- Voltage controlled voltage source
  - (VCVS)
- Current controlled voltage source
  - (CCVS)
- Voltage controlled current source
  - (VCCS)
- Current controlled current source
  - (CCCS)



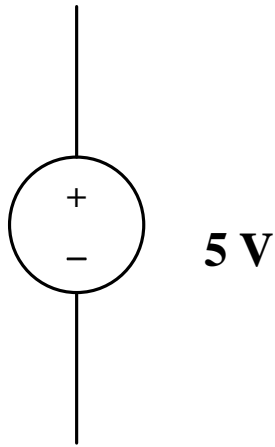
# Summary

- Dependent sources are voltage or current sources whose output is a function of another parameter in the circuit.
  - Voltage controlled voltage source (VCVS)
  - Current controlled current source (CCCS)
  - Voltage controlled current source (VCCS)
  - Current controlled voltage source (CCVS)
- Dependent sources only produce a voltage or current when an independent voltage or current source is in the circuit.
- Dependent sources are treated like independent sources when using nodal or mesh analysis, but **not** with superposition.


Independent and dependent voltage and current sources can be represented as




Independent voltage source

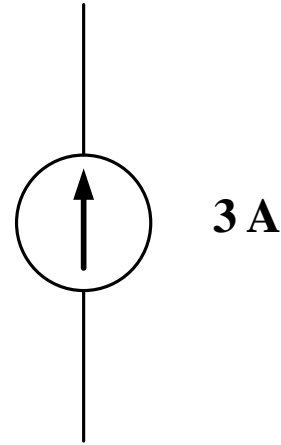

Independent current source

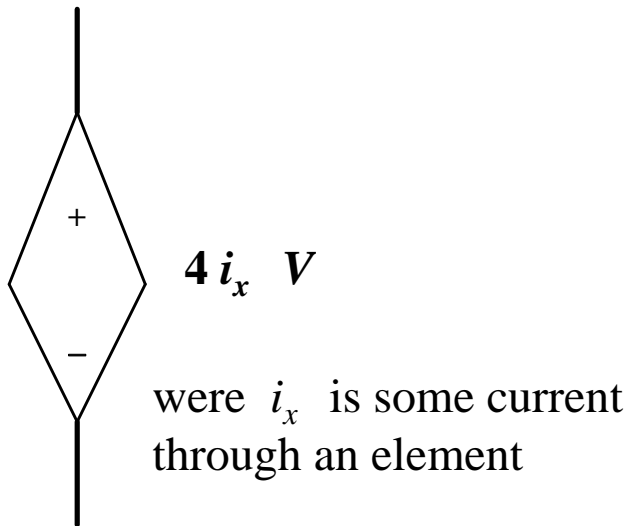


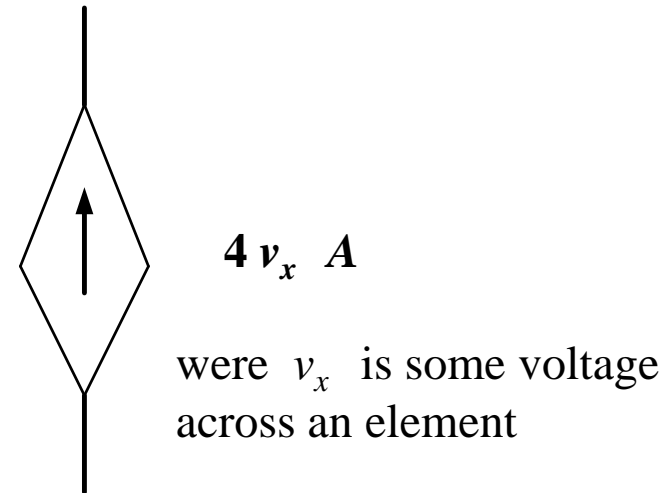**Dependent voltage source**  
**Voltage depends on current**



**Dependent current source**  
**Current depends on voltage**


The dependent sources can be also as

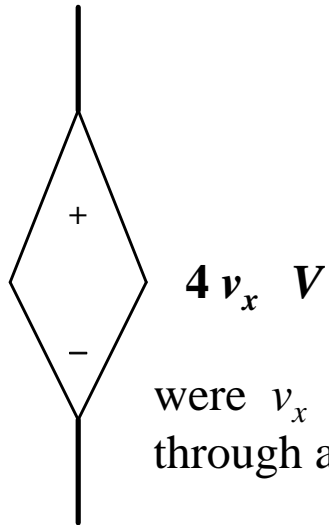

$$4 v_x \text{ V}$$

where  $v_x$  is some current  
through an element

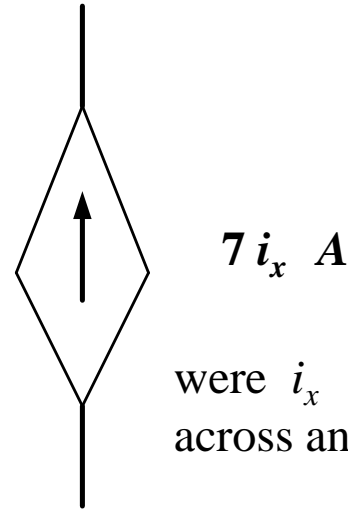**Dependent voltage source**  
**Voltage depend on voltage**



$$7 i_x \text{ A}$$

where  $i_x$  is some voltage  
across an element

**Dependent current source**  
**Current depend on current**



First we shall discuss about the analysis of DC circuit. The voltage across an element is denoted as  $E$  or  $V$ . The current through the element is  $I$ .

Conductor is used to carry current. When a voltage is applied across a conductor, current flows through the conductor. If the applied voltage is increased, the current also increases. The voltage current relationship is shown in Fig. 1.

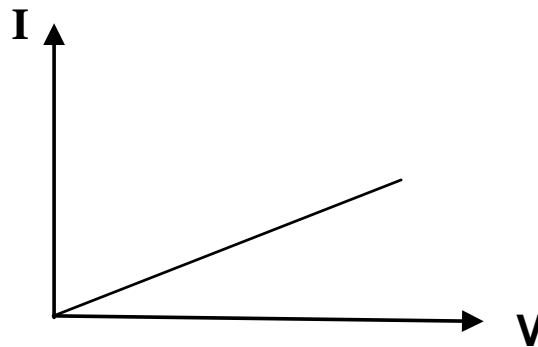


Fig. 1 Voltage – current relationship


It is seen that  $I \propto V$ . Thus we can write

$$I = G V \quad (1)$$


where  $G$  is called the conductance of the conductor.

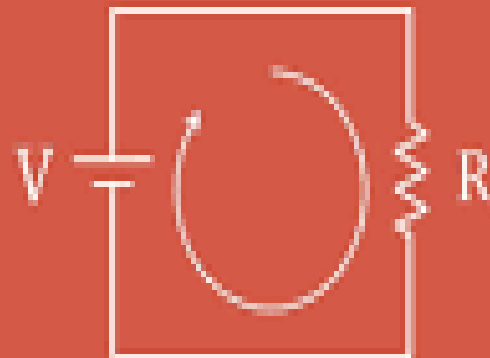
## Definition of Ohm's law

The current in an electrical circuit is directly proportional to the applied voltage and inversely proportional to the resistance.



# OHM'S LAW

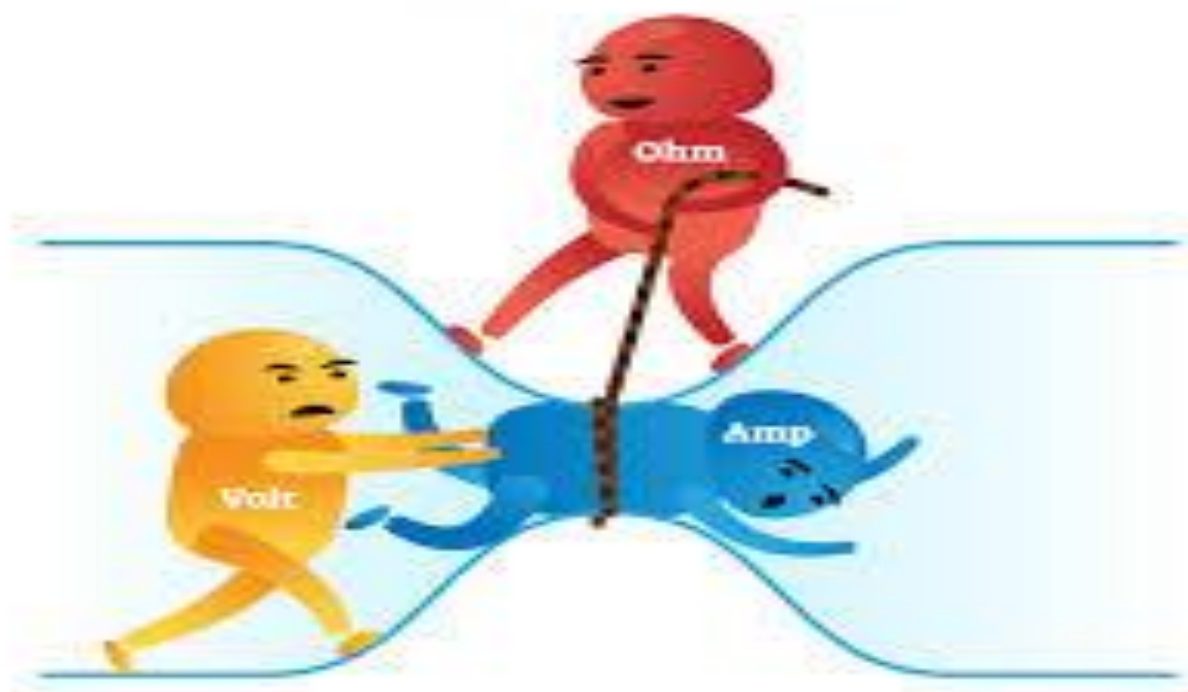

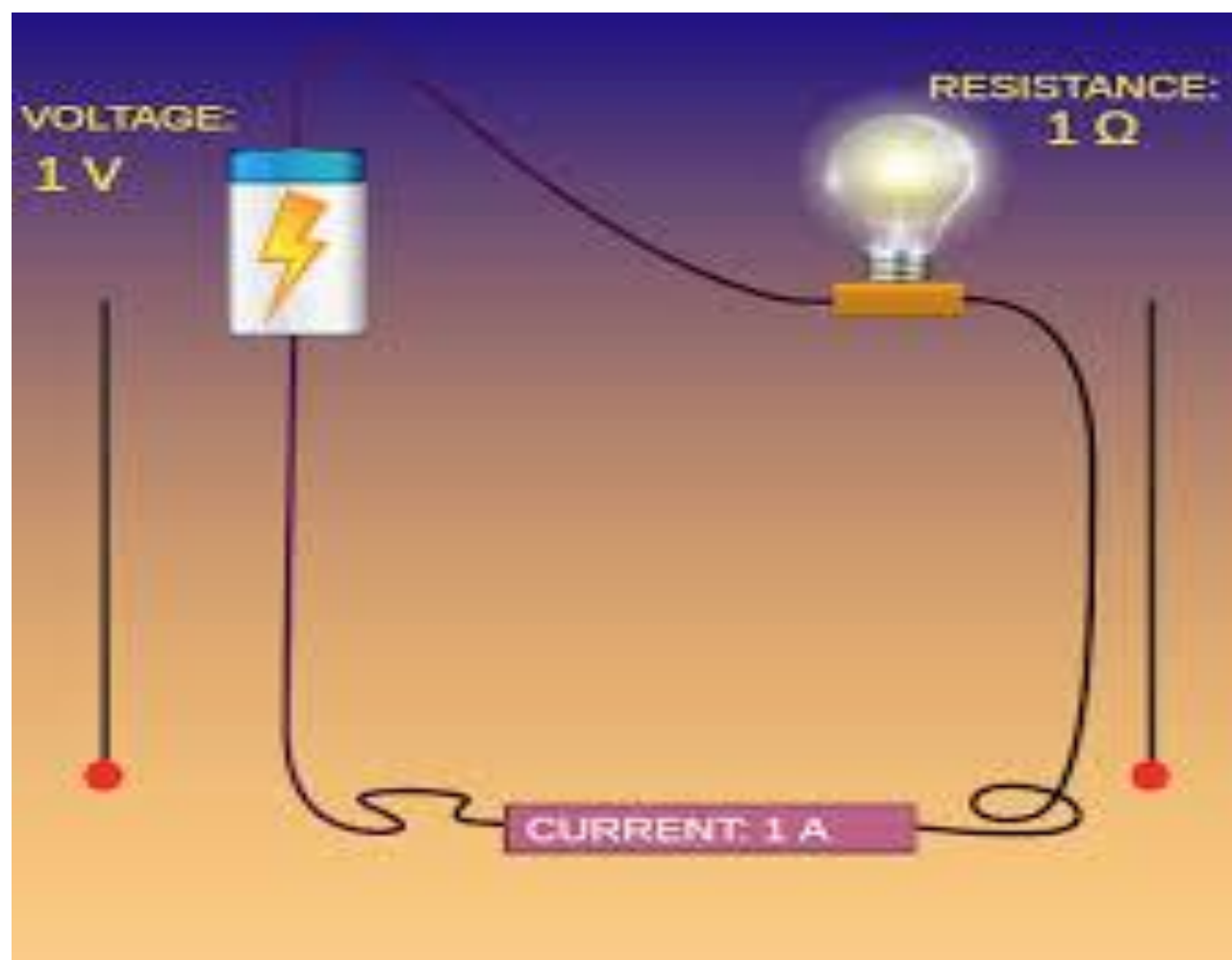

**Very often we are more interested on RESISTANCE, R of the conductor, than the conductance of the conductor. Resistance is the opposing property of the conductor and it is the reciprocal of the conductance, Thus**

$$\mathbf{R = \frac{1}{G} \quad or \quad G = \frac{1}{R}} \quad (2)$$

**Therefore**

$$\mathbf{I = \frac{V}{R}} \quad (3)$$

**The above relationship is known as OHM's law. Thus Ohm law can be stated as the current flows through a conductor is the ratio of the voltage across the conductor and its resistance. Ohm's law can also be written as**

$$\mathbf{V = R I} \quad (4)$$

$$\mathbf{R = \frac{V}{I}} \quad (5)$$

**The resistance of a conductor is directly proportional to its length, inversely proportional to its area of cross section. It also depends on the material of the conductor. Thus**

$$R = \rho \frac{\ell}{A} \quad (6)$$

**where  $\rho$  is called the specific resistance of the material by which the conductor is made of. The unit of the resistance is Ohm and is represented as  $\Omega$ . Resistance of a conductor depends on the temperature also. The power consumed by the resistor is given by**

$$P = V I \quad (7)$$

**When the voltage is in volt and the current is in ampere, power will be in watt. Alternate expression for power consumed by the resistors are given below.**

$$P = R I \times I = I^2 R \quad (8)$$

$$P = V \times \frac{V}{R} = \frac{V^2}{R} \quad (9)$$

## Kirchhoff's current law

Kirchhoff's currents law states that the algebraic sum of element current meeting at a junction is zero.

Consider a junction P wherein four elements, carrying currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ , are meeting as shown in Fig. 2.

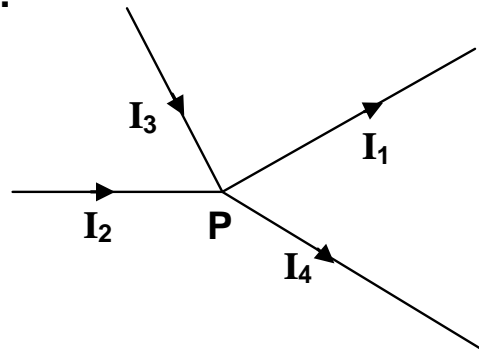


Fig. 2 Currents meeting at a junction

Note that currents  $I_1$  and  $I_4$  are flowing out from the junction while the currents  $I_2$  and  $I_3$  are flowing into the junction. According to KCL,

$$I_1 - I_2 - I_3 + I_4 = 0 \quad (10)$$

The above equation can be rearranged as

$$I_1 + I_4 = I_2 + I_3 \quad (11)$$

From equation (11), KCL can also be stated as at a junction, the sum of element currents that flows out is equal to the sum of element currents that flows in.

## Kirchhoff's voltage law

Kirchhoff's voltage law states that the algebraic sum of element voltages around a closed loop is zero.

Consider a closed loop in a circuit wherein four elements with voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$ , are present as shown in Fig. 3.

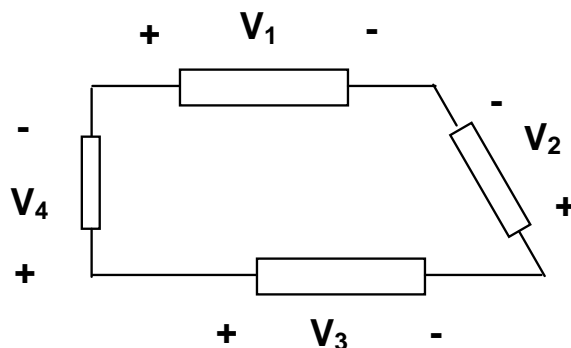


Fig. 3 Voltages in a closed loop

Assigning positive sign for voltage drop and negative sign for voltage rise, when the loop is traced in clockwise direction, according to KVL

$$V_1 - V_2 - V_3 + V_4 = 0 \quad (12)$$

The above equation can be rearranged as

$$V_1 + V_4 = V_2 + V_3 \quad (13)$$

From equation (13), KVL can also be stated as, in a closed loop, the sum of voltage drops is equal to the sum of voltage rises in that loop.



## Resistors connected in series

Two resistors are said to be connected in series when there is only one common point between them and no other element is connected in that common point. Resistors connected in series carry same current. Consider three resistors  $R_1$ ,  $R_2$  and  $R_3$  connected in series as shown in Fig. 4. With the supply voltage of  $E$ , voltages across the three resistors are  $V_1$ ,  $V_2$  and  $V_3$ .

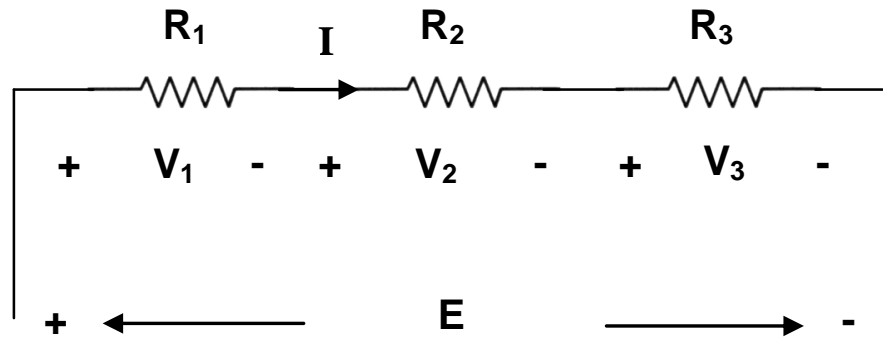


Fig. 4 Resistors connected in series

As per Ohm's law

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$V_3 = R_3 I$$



(14)

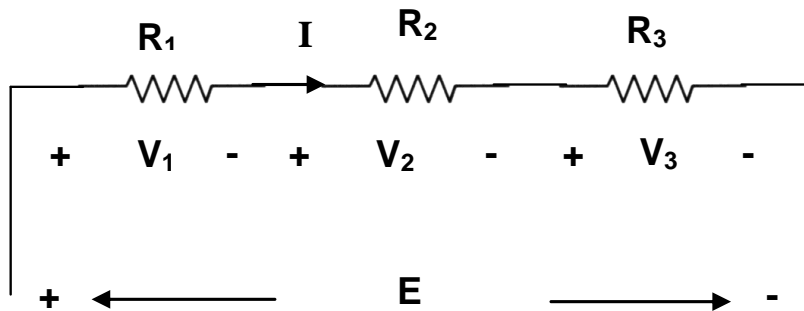


Fig. 4 Resistors connected in series

As per Ohm's law

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$V_3 = R_3 I$$

Applying KVL,

$$E = V_1 + V_2 + V_3 \quad (15)$$

$$= (R_1 + R_2 + R_3) I = R_{eq} I \quad (16)$$

Thus for the circuit shown in Fig. 4,

$$E = R_{eq} I \quad (17)$$

where  $E$  is the circuit voltage,  $I$  is the circuit current and  $R_{eq}$  is the equivalent resistance. Here


$$R_{eq} = R_1 + R_2 + R_3 \quad (18)$$

This is true when two or more resistors are connected in series. When  $n$  numbers of resistors are connected in series, the equivalent resistor is given by

$$R_{eq} = R_1 + R_2 + \dots + R_n \quad (19)$$
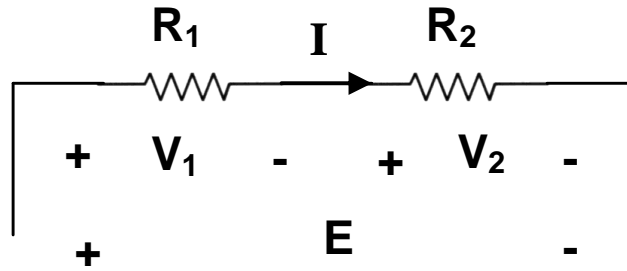
## Voltage division rule

Consider two resistors connected in series. Then



$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$E = (R_1 + R_2) I \text{ and hence } I = E / (R_1 + R_2)$$

Total voltage of  $E$  is dropped in two resistors. Voltage across the resistors are given by

$$V_1 = \frac{R_1}{R_1 + R_2} E \quad \text{and} \quad (20)$$

$$V_2 = \frac{R_2}{R_1 + R_2} E \quad (21)$$

## Resistors connected in parallel

Two resistors are said to be connected in parallel when both are connected across same pair of nodes. Voltages across resistors connected in parallel will be equal.

Consider two resistors  $R_1$  and  $R_2$  connected in parallel as shown in Fig. 5.


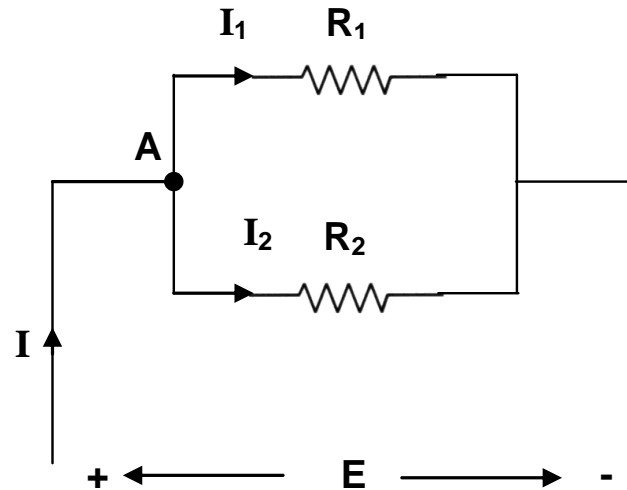


Fig. 5 Resistors connected in parallel

As per Ohm's law,

$$\left. \begin{aligned} I_1 &= \frac{E}{R_1} \\ I_2 &= \frac{E}{R_2} \end{aligned} \right\}$$

(22)

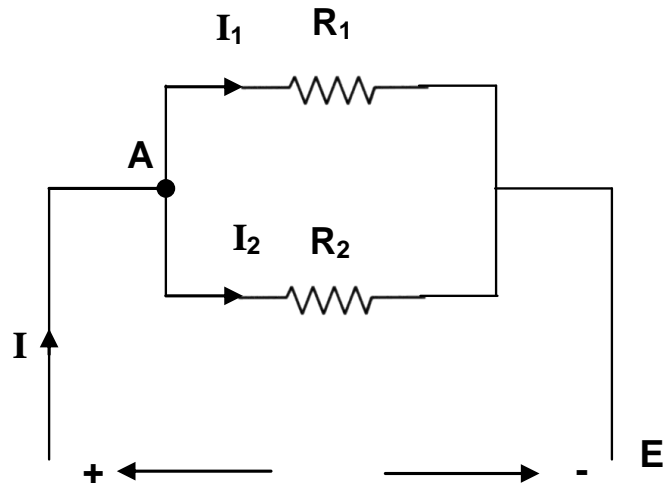

As per Ohm's law

$$I_1 = \frac{E}{R_1}$$

$$I_2 = \frac{E}{R_2}$$

Applying KCL at node A

$$I = I_1 + I_2 = E \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E}{R_{eq}} \quad (23)$$

Thus for the circuit shown in Fig. 5

$$I = \frac{E}{R_{eq}} \quad (24)$$

where E is the circuit voltage, I is the circuit current and  $R_{eq}$  is the equivalent resistance. Here

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (25)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (25)$$

From the above  $\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$

Thus  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad (26)$

When n numbers of resistors are connected in parallel, generalizing eq. (25),  $R_{eq}$  can be obtained from

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \quad (27)$$

## Current division rule

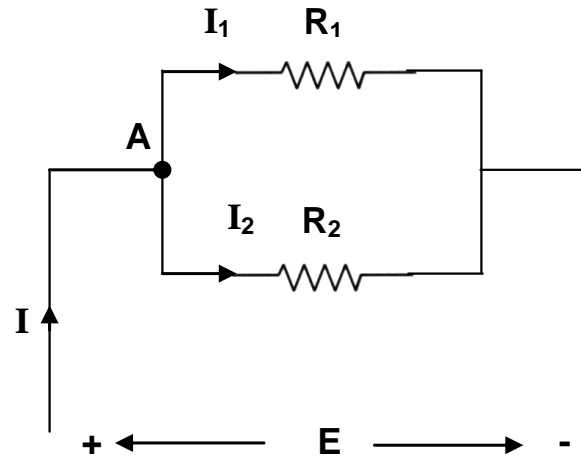


Fig. 5 Resistors connected in parallel

Referring to Fig. 5, it is noticed the total current gets divided as  $I_1$  and  $I_2$ . The branch currents are obtained as follows.

From eq. (23)

$$E = \frac{R_1 R_2}{R_1 + R_2} I \quad (29)$$


Substituting the above in eq. (22)

$$\left. \begin{aligned} I_1 &= \frac{R_2}{R_1 + R_2} I \\ I_2 &= \frac{R_1}{R_1 + R_2} I \end{aligned} \right\} \quad (30)$$

### Example

Three resistors  $10\Omega$ ,  $20\Omega$  and  $30\Omega$  are connected in series across  $100\text{ V}$  supply. Find the voltage across each resistor.

### Solution

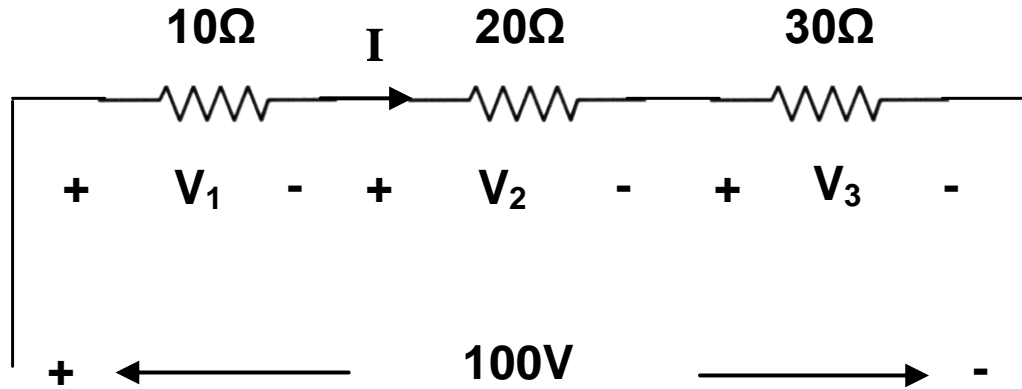

$$\text{Current } I = 100 / (10 + 20 + 30) = 1.6667 \text{ A}$$

$$\text{Voltage across } 10\Omega = 10 \times 1.6667 = 16.67 \text{ V}$$

$$\text{Voltage across } 20\Omega = 20 \times 1.6667 = 33.33 \text{ V}$$


$$\text{Voltage across } 30\Omega = 30 \times 1.6667 = 50 \text{ V}$$



### Example

Two resistors of  $4\Omega$  and  $6\Omega$  are connected in parallel. If the supply current is  $30\text{ A}$ , find the current in each resistor.

### Solution

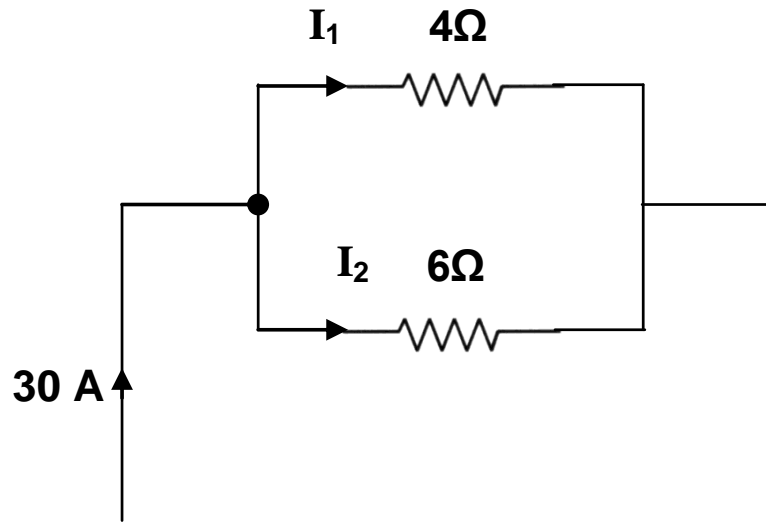

Using the current division rule

$$\text{Current through } 4\Omega = \frac{6}{4 + 6} \times 30 = 18\text{ A}$$

$$\text{Current through } 6\Omega = \frac{4}{4 + 6} \times 30 = 12\text{ A}$$

### Example

Four resistors of 2 ohms, 3 ohms, 4 ohms and 5 ohms respectively are connected in parallel. What voltage must be applied to the group in order that the total power of 100 W is absorbed?

### Solution

Let  $R_T$  be the total equivalent resistor. Then

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{3} + \frac{1}{4} + \frac{1}{5} = \frac{60 + 40 + 30 + 24}{120} = \frac{154}{120}$$

$$\text{Resistance } R_T = \frac{120}{154} = 0.7792 \, \Omega$$

Let  $E$  be the supply voltage. Then total current taken =  $E / 0.7792 \, \text{A}$



$$\text{Thus } \left( \frac{E}{0.7792} \right)^2 \times 0.7792 = 100 \text{ and hence } E^2 = 100 \times 0.7792 = 77.92$$

$$\text{Required voltage} = \sqrt{77.92} = 8.8272 \, \text{V}$$

### Example

When a resistor is placed across a 230 V supply, the current is 12 A. What is the value of the resistor that must be placed in parallel, to increase the load to 16 A

### Solution

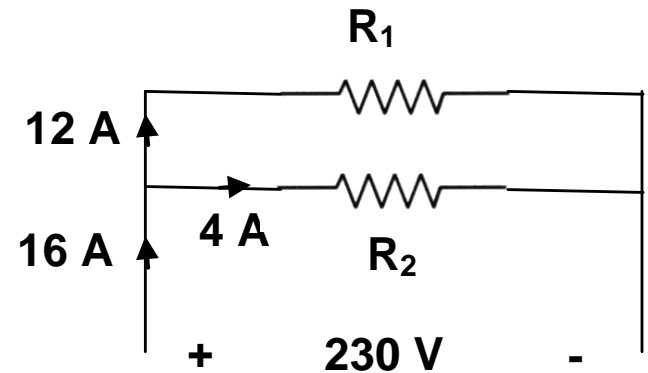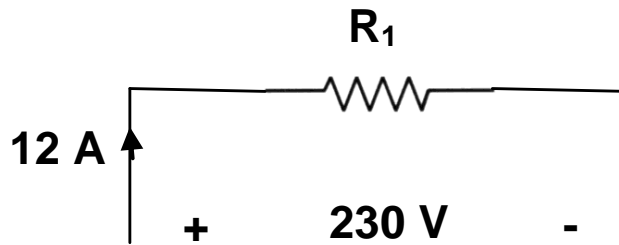



To make the load current 16 A, current through the second resistor =  $16 - 12 = 4$  A

Value of second resistor  $R_2 = 230/4 = 57.5 \Omega$

### Example

A  $50\ \Omega$  resistor is in parallel with a  $100\ \Omega$  resistor. The current in  $50\ \Omega$  resistor is  $7.2\text{ A}$ . What is the value of third resistor to be added in parallel to make the line current as  $12.1\text{ A}$ ?

### Solution

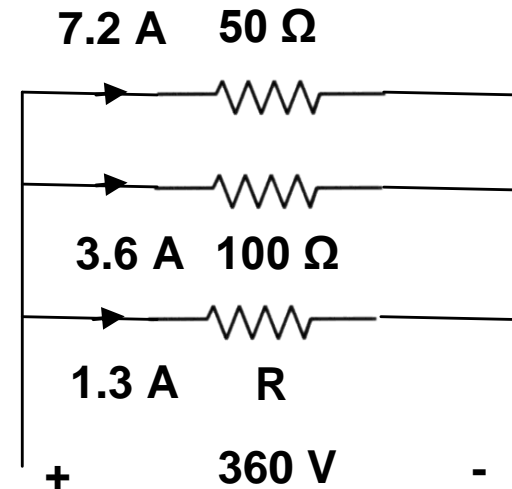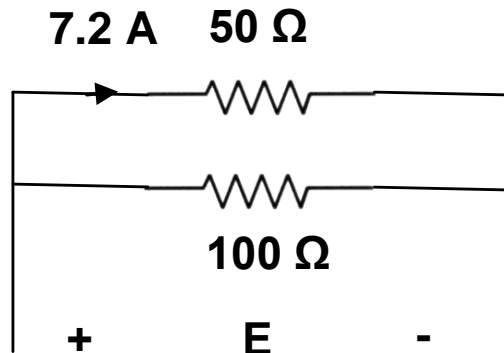


Supply voltage  $E = 50 \times 7.2 = 360\text{ V}$

Current through  $100\ \Omega = 360/100 = 3.6\text{ A}$

When the line current is  $12.1\text{ A}$ , current through third resistor  $= 12.1 - (7.2 + 3.6)$   
 $= 1.3\text{ A}$


Value of third resistor  $= 360/1.3 = 276.9230\ \Omega$

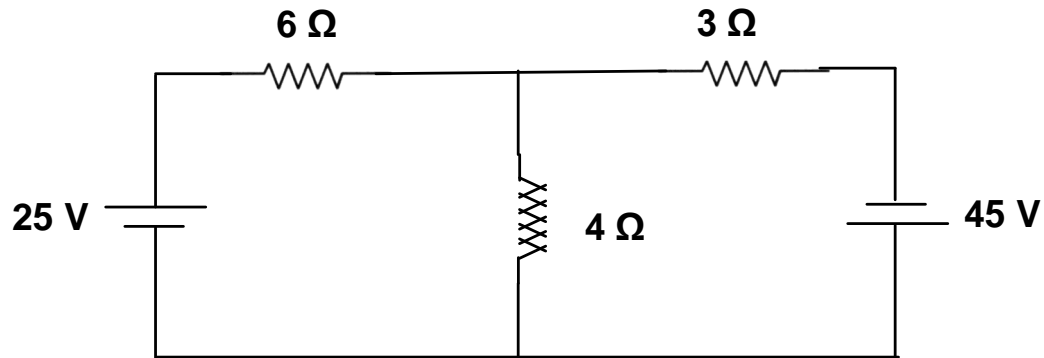
Using Kirchhoff's laws, find the current in various resistors in the circuit shown.


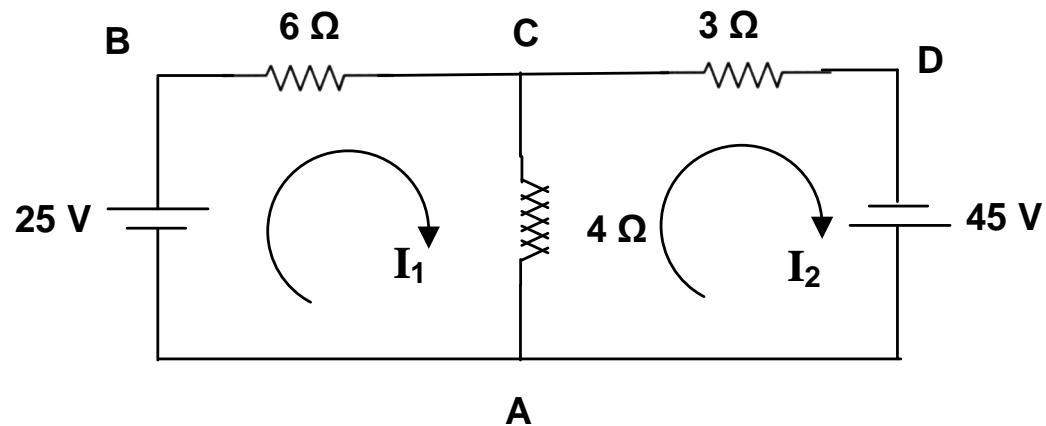
### Solution

Let the loop current be  $I_1$  and  $I_2$



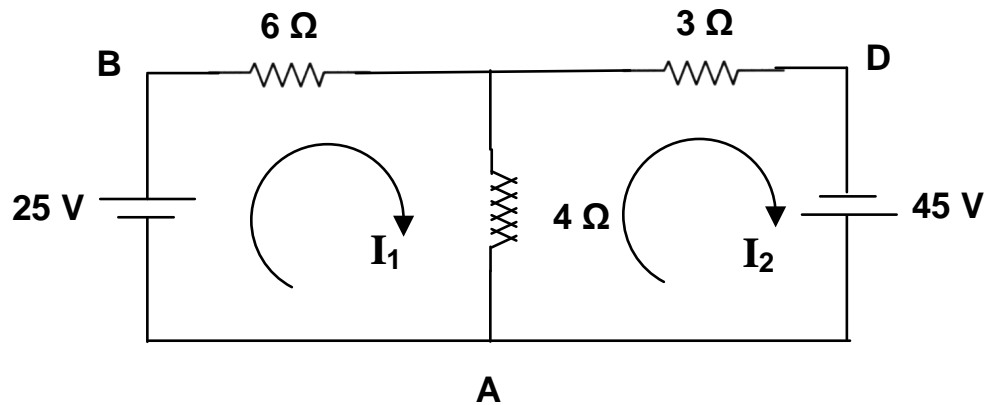

Considering the loop ABCA, KVL yields

$$6 I_1 + 4 (I_1 - I_2) - 25 = 0$$

For the loop CDAC, KVL yields

$$3 I_2 - 45 + 4 (I_2 - I_1) = 0$$

$$\text{Thus } 10 I_1 - 4 I_2 = 25$$

$$- 4 I_1 + 7 I_2 = 45$$


On solving the above  $I_1 = 6.574 \text{ A}$ ;  $I_2 = 10.1852 \text{ A}$

$$\text{Current in } 4\Omega \text{ resistor} = I_1 - I_2 = 6.574 - 10.1852 = - 3.6112 \text{ A}$$

Thus the current in 4Ω resistor is 3.6112 A from A to C


$$\text{Current in } 6 \Omega \text{ resistor} = 6.574 \text{ A}; \text{ Current in } 3 \Omega \text{ resistor} = 10.1852 \text{ A}$$

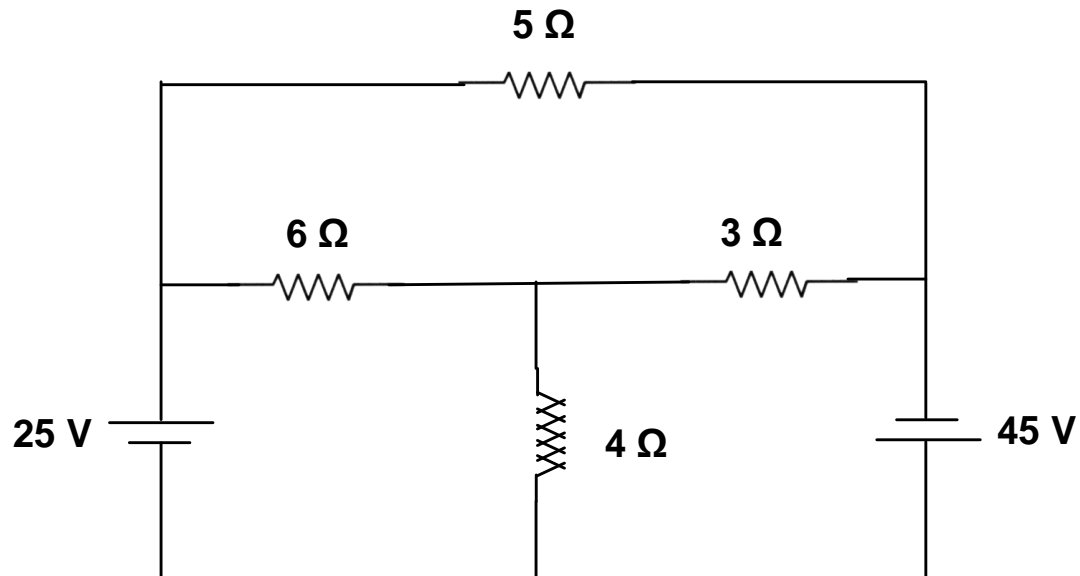Find the current in  $5\ \Omega$  resistor in the circuit shown.


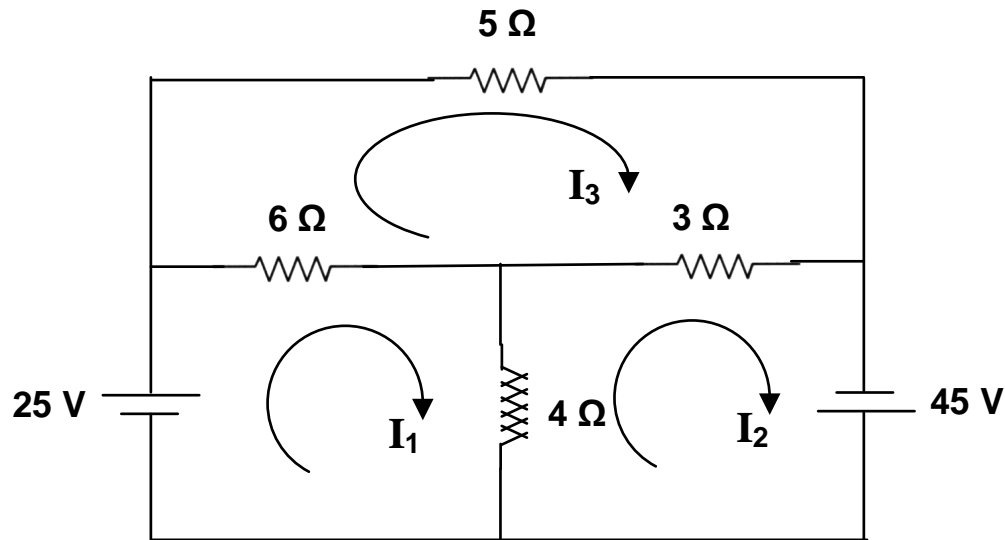
## Solution

Let the loop current be  $I_1$ ,  $I_2$  and  $I_3$ .



Three loops equations are:

$$6 (I_1 - I_3) + 4 (I_1 - I_2) - 25 = 0$$

$$4 (I_2 - I_1) + 3 (I_2 - I_3) - 45 = 0$$

$$5 I_3 + 3 (I_3 - I_2) + 6 (I_3 - I_1) = 0$$

On solving

Current in 5  $\Omega$  resistor,  $I_3 = 14 \text{ A}$