

3-phase AC circuits:-

→ 3 ϕ system is a combination of 3 single phase systems.

→ In a balanced 3 ϕ system, 3 voltages in phase by 120° electrical from each other in a particular sequence and they have equal magnitudes.

Advantages of 3 ϕ system:-

- (i) More efficient than 1 ϕ system.
- (ii) Transmission of same power, 3 ϕ circuits require less conductor material than 1 ϕ system.
- (iii) 3 ϕ motors self starting but 1 ϕ motors are not self starting.
- (iv) 1 ϕ motors producing pulsating torque, but 3 ϕ motor produces uniform torque.
- (v) Generation, transmission & distribution of 3 ϕ system is cheaper.


→ Consider 3 coils are R, Y, B which is displaced by 120° each other. According to Faraday's law of electromagnetic induction EMF induced in 3 coils are,

$$V_R = V_m \sin \omega t,$$


$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ).$$

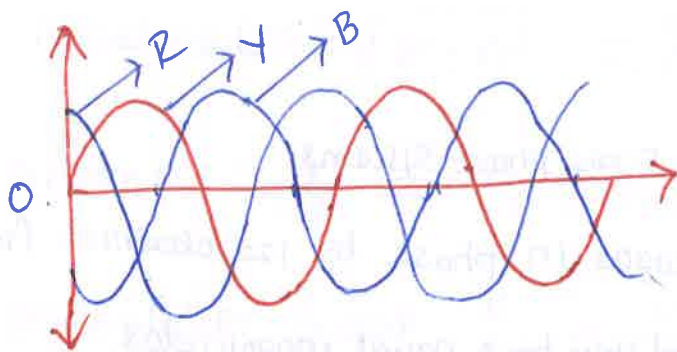} → All these 3 emf have the same magnitude Amplitude Time period, frequency, but the starting and ending points are different.



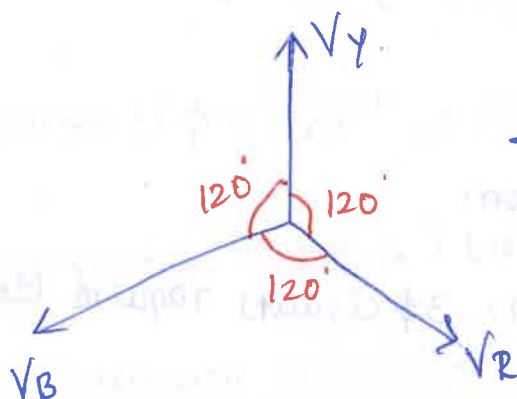→ In case emf induced in R phase is V_R be taken as reference, V_Y lags behind by 120° from V_R and V_B lags 240° from the V_R .




→ In order in which the different phasors reach their respective maximum and minimum values is known as Phase sequence.

→ Which indicates the rotation of phasors in a particular direction.

Three phase connections :-

Star connection :-

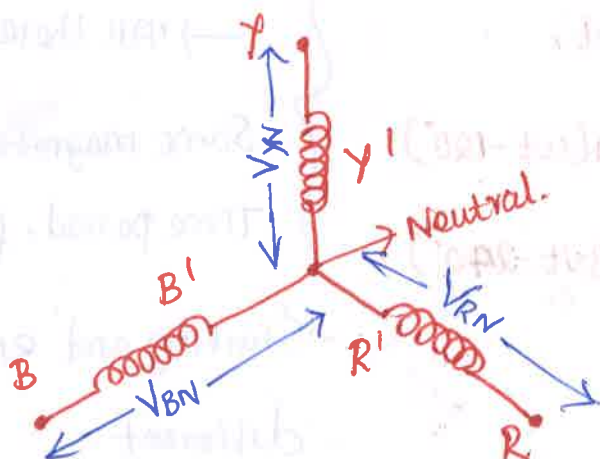→ In a star connection, the similar ends of different coils connected together to form a ~~new~~ neutral point.



→ Voltage and current induced in each phase is known as phase voltage and phase current (I_{ph}).
(V_{ph})

→ potential different between 2 phase is known as line voltage (V_L).

from the diagram line voltages are,

$$V_L = \sqrt{3} V_{ph}$$

→ The current passing through any 2 phases are remains the same thus,

i.e., Line current = phase current.

$$I_L = I_{ph}$$

Power = 3 x phase power

$$= 3 (V_{ph} I_{ph} \cos \phi) = 3 \frac{V_L}{\sqrt{3}} \cdot I_L \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi \text{ Watts}$$

Delta connection:-

→ If the 3 windings are connected at end of the one phase to the start of another. we get closed winding is known as delta connection.

→ In this case, there is only one winding is included between any two phases. hence, the voltage between 2 phase is equal to phase voltage.

Q.

$$V_L = V_{ph} = V_{RY} = V_{BR} = V_{YB}$$

Thus, $I_L = \sqrt{3} I_{ph}$.

power = 3 x phase power $\Rightarrow 3 V_{ph} I_{ph} \cos \phi$.

$$= 3 V_L \left(\frac{I_L}{\sqrt{3}} \right) \cos \phi = \sqrt{3} V_L I_L \cos \phi.$$

$$P = \sqrt{3} V_L I_L \cos \phi \text{ Watts}$$

1) An inductive coil takes 10A and dissipates 1000W. When connected to a supply at 250V, 25Hz. Calculate the impedance, the effective resistance, the reactance, the inductance & the power factor.

Soln:-

$I = 10A$, $p = 1000W$ (actual power), $V = 250V$, $f = 25Hz$.

Inductive coil will also have certain resistance, so, it is equivalent to an R-L circuit.

$$\text{power} = VI \cos \phi \Rightarrow I^2 R = 1000$$

$$(10)^2 \times R = 1000$$

$$R = \frac{1000}{100} = 10 \Omega.$$

$$\text{impedance } (Z) = \frac{V}{I} = \frac{250}{10} = 25 \Omega.$$

$$= \sqrt{R^2 + X_L^2}, \quad X_L = \sqrt{Z^2 - R^2} = 22.91 \Omega.$$

$$X_L = \omega L = 2\pi fL$$

$$22.91 = 2\pi fL \xrightarrow{25}$$

$$22.91 = 2\pi \times 25 \times L, \quad \boxed{L = 0.146 H.}$$

$$\text{Power factor} \Rightarrow \cos \phi = \frac{R}{Z} = \frac{10}{25} = 0.4 \text{ lagging.}$$

Otherwise,

$$P = VI \cos \phi$$

$$1000 = 250 \times 10 \times \cos \phi$$

$$\cos \phi = 0.4 \text{ lagging}$$