
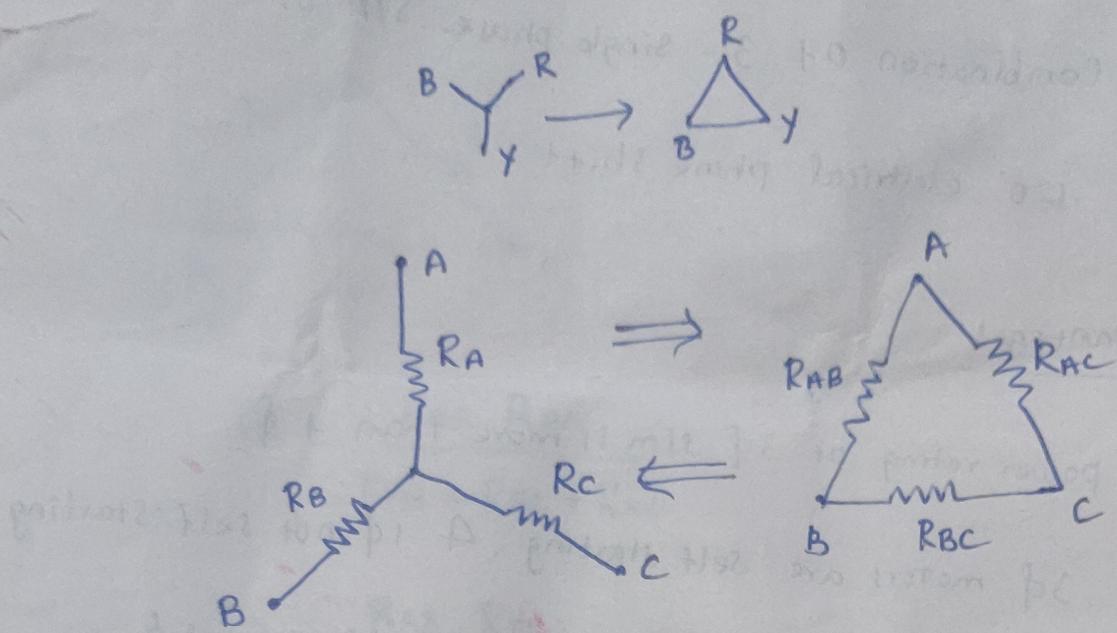


## Star - Delta Transformation

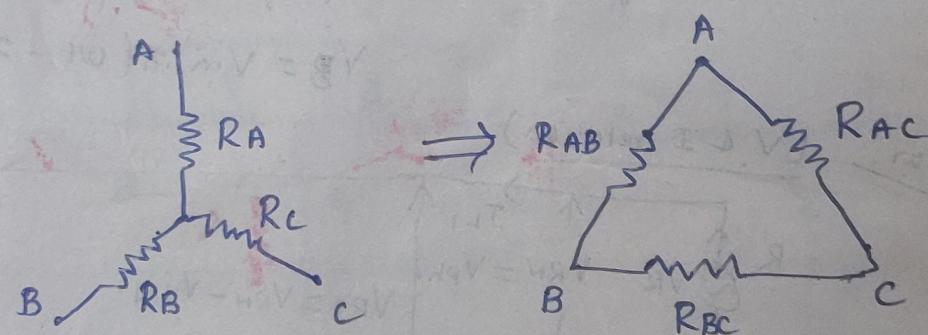

→ For circuit reduction using this Star - Delta transformation.

### Star - Delta :-




$$R_{AB} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_C}$$

$$R_{AC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_B}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_A}$$

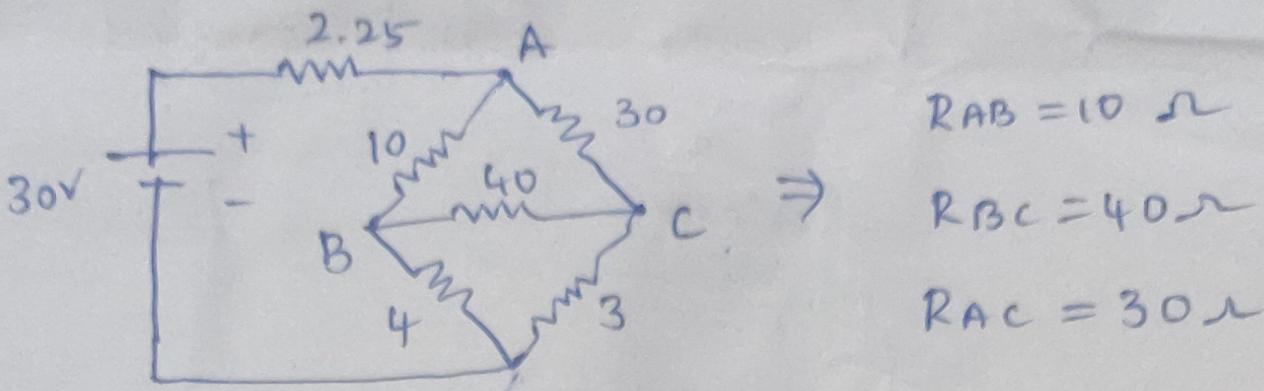2) Find the source current for the given circuit.



$$R_{AB} = 10 \Omega$$



$$R_{BC} = 40 \Omega$$

$$R_{AC} = 30 \Omega$$

$$R_A = \frac{R_{AB} \cdot R_{AC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{10 \times 30}{10 + 40 + 30} = 3.75 \Omega$$

$$R_B = \frac{R_{BC} \cdot R_{AB}}{R_{AB} + R_{BC} + R_{CA}} = \frac{40 \times 10}{10 + 40 + 30} = 5 \Omega$$

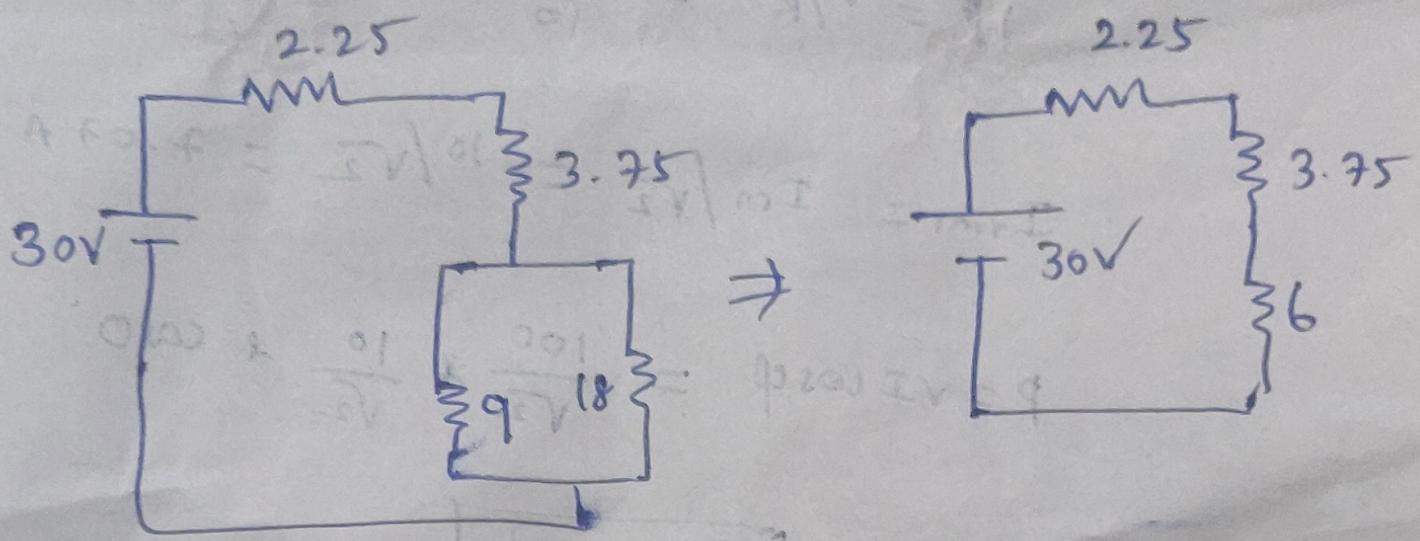
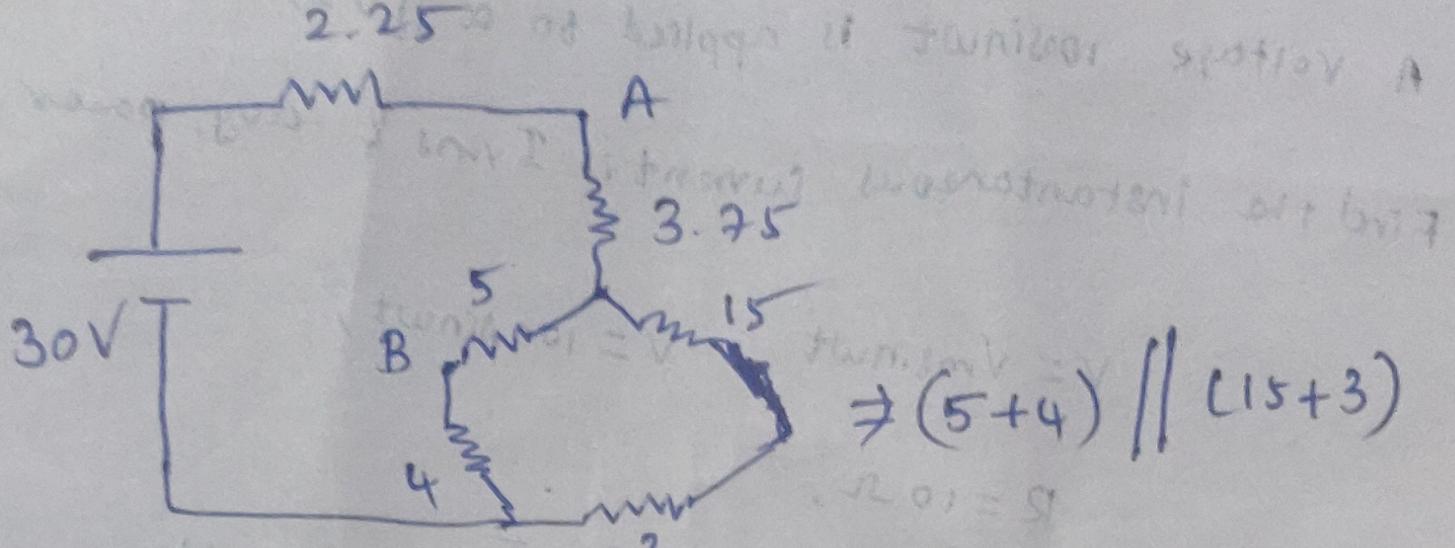
$$R_C = \frac{R_{AC} * R_{BC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{30 * 40}{10 + 40 + 30} = 15 \Omega$$



$$30V \xrightarrow{2.25} \frac{I}{12} \Rightarrow I = \frac{V}{R} = \frac{30}{12}$$


$$I = 2.5 A$$

1) Find R-equivalent for given circuit.

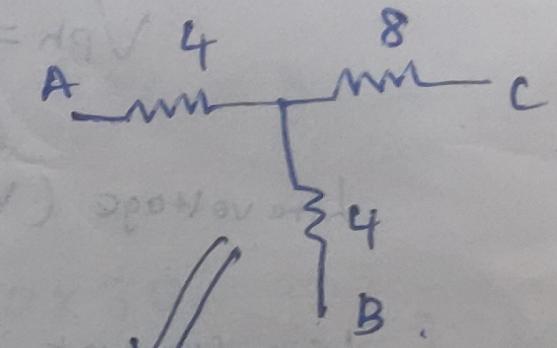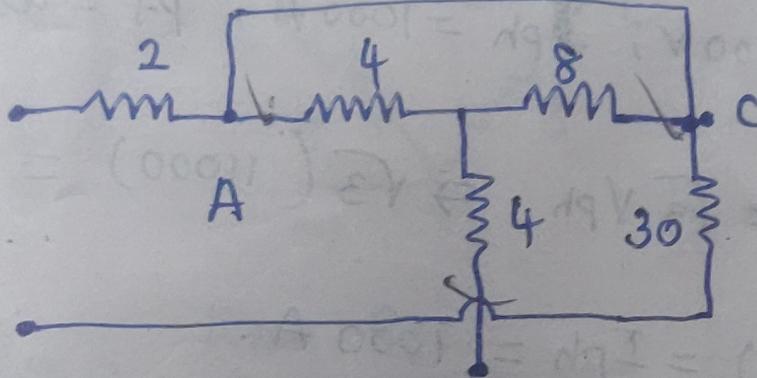

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_C}$$



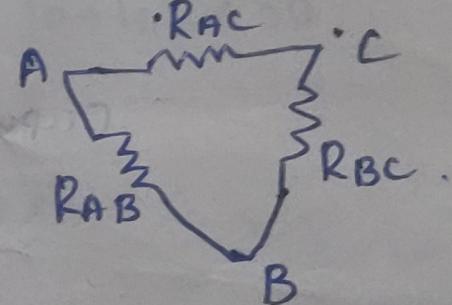
$$= \frac{(4 \times 4) + (4 \times 8) + (4 \times 8)}{8}$$



$$R_{AB} = 80/8, \boxed{R_{AB} = 10\Omega}$$

$$R_{BC} = 80/4, \boxed{20\Omega}$$

$$R_{AC} = 20\Omega$$

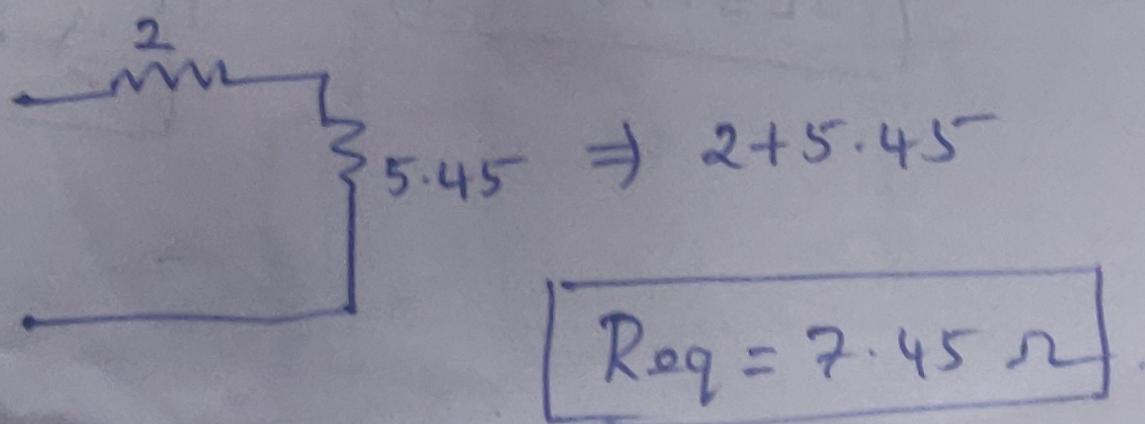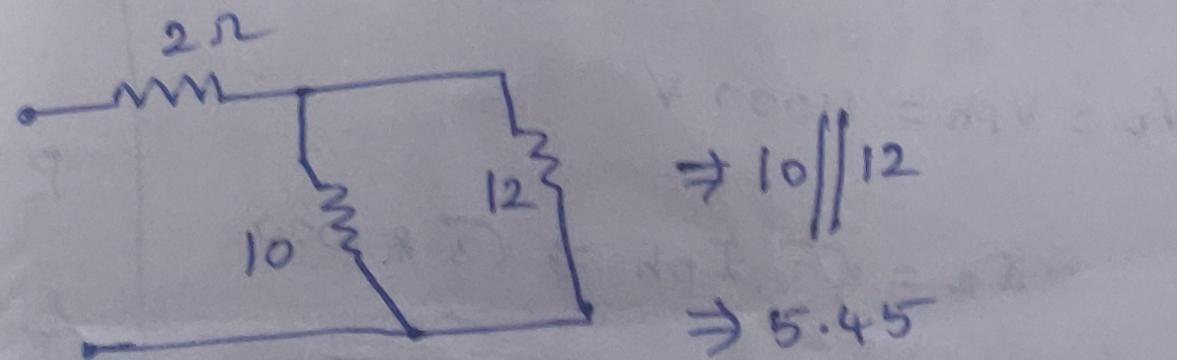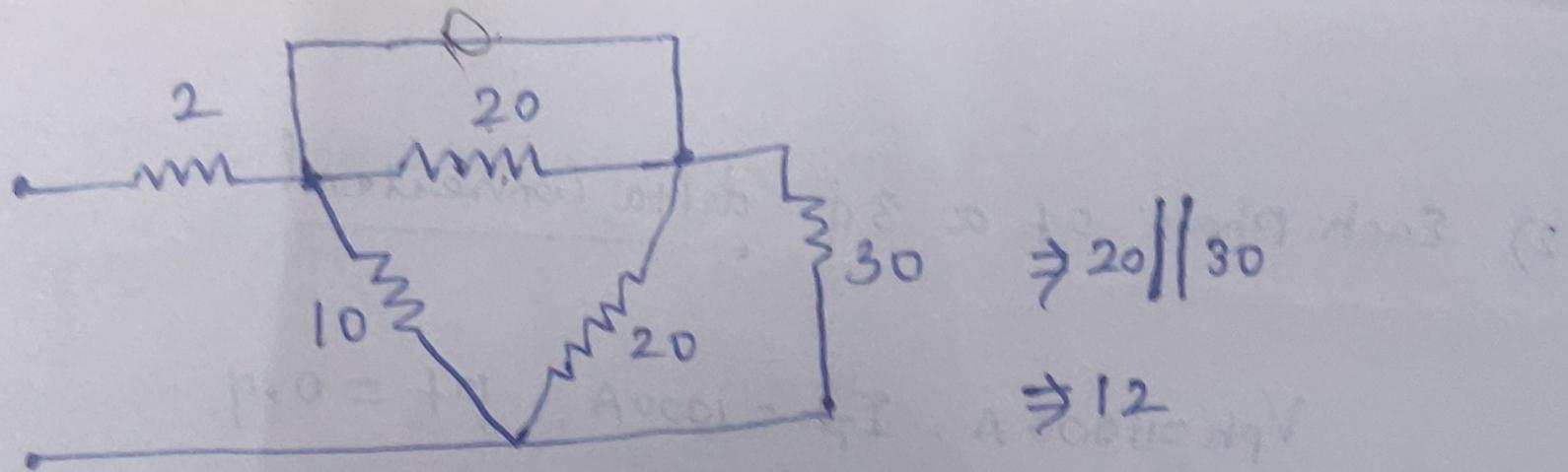

1) Each phase of a 3φ star connected alternator produces a voltage of 11000 V & current of 1000 A at power factor of 0.9. Find the line voltage, line current & total capacity of the alternator.

$$V_{ph} = 11000 \text{ V}, I_{ph} = 1000 \text{ A}, Pf = \cos\phi = 0.9$$

$$\text{Line voltage } (V_L) = \sqrt{3} V_{ph} \Rightarrow \sqrt{3} (11000) = 19052.5 \text{ V}$$

$$\text{Line current } (I_L) = I_{ph} = 1000 \text{ A}$$

$$\text{Capacity of power } (P_L) = \sqrt{3} V_L I_L \cos\phi$$

$$= \sqrt{3} (19052.5) (1000) \times (0.9)$$

$$P_L = 29.7 \text{ MW}$$

1. A voltage  $100\sin\omega t$  is applied to a  $10-\Omega$  resistor.

Find the instantaneous current,  $I_{rms}$  & avg. power.

$$(E+iR) \parallel (P+Z) \Rightarrow V = \sqrt{V_{ms}^2 + i^2 R^2} = \sqrt{V_{ms}^2 + (V/R)^2 R^2} = \sqrt{V_{ms}^2 + V^2} = \sqrt{V_{ms}^2(1 + 1/\tan^2 \theta)} = V_{ms} \csc \theta$$

$$R = 10 \Omega,$$

$$i_f = V/R = \frac{100 \sin\omega t}{10} = 10 \sin\omega t.$$

$$I_{rms} = I_m / \sqrt{2} = 10 / \sqrt{2} = 7.07 A$$

$$P = VI \cos\phi = \frac{100}{\sqrt{2}} * \frac{10}{\sqrt{2}} * \cos 0^\circ$$

$$P = 500 W$$